Introduction to CMOS VLSI Design

Lecture 1: Circuits & Layout

Outline


- □ A Brief History
- CMOS Gate Design
- Pass Transistors
- CMOS Latches & Flip-Flops
- Standard Cell Layouts
- ☐ Stick Diagrams

A Brief History

- ☐ 1958: First integrated circuit
 - Flip-flop using two transistors
 - Built by Jack Kilby at Texas Instruments
- **2**003
 - Intel Pentium 4 μprocessor (55 million transistors)
 - 512 Mbit DRAM (> 0.5 billion transistors)
- ☐ 53% compound annual growth rate over 45 years
 - No other technology has grown so fast so long
- Driven by miniaturization of transistors
 - Smaller is cheaper, faster, lower in power!
 - Revolutionary effects on society

Annual Sales

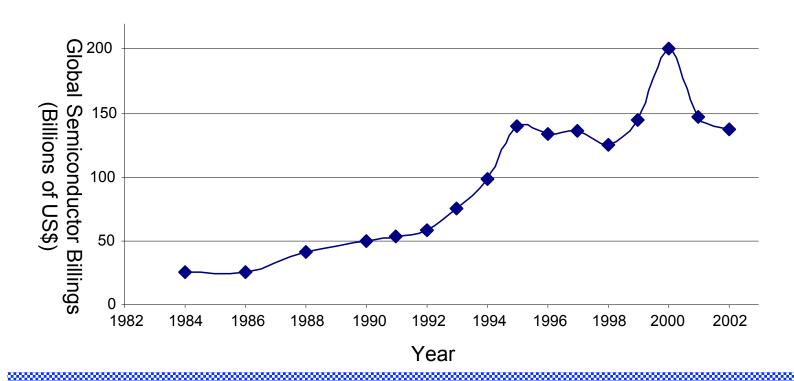
- □ 10¹⁸ transistors manufactured in 2003
 - 100 million for every human on the planet



Invention of the Transistor

電晶體 原本是 真空管。但太耗電

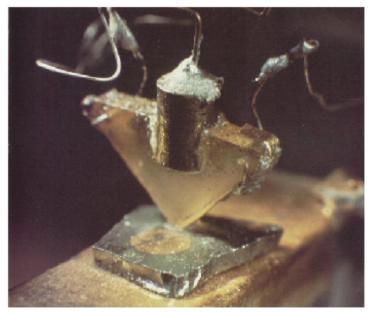- □ Vacuum tubes ruled in first half of 20th century Large, expensive, power-hungry, unreliable
- ☐ 1947: first point contact transistor
 - John Bardeen and Walter Brattain at Bell Labs
 - Read Crystal Fireby Riordan, Hoddeson




Transistor Types

兩極 的 電晶體 二極體

Bipolar transistors




– npn or pnp silicon structure

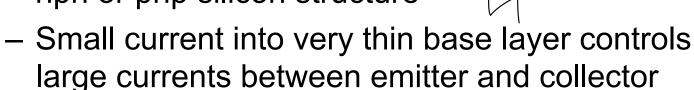


- Base currents limit integration density
- Metal Oxide Semiconductor Field Effect Transistors
 - nMOS and pMOS MOSFETS 是用电場成应
 - Voltage applied to insulated gate controls current between source and drain
 - Low power allows very high integration

MOS Integrated Circuits

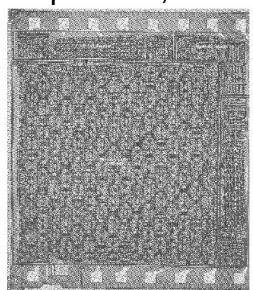- ☐ 1970's processes usually had only nMOS transistors
 - Inexpensive, but consume power while idle



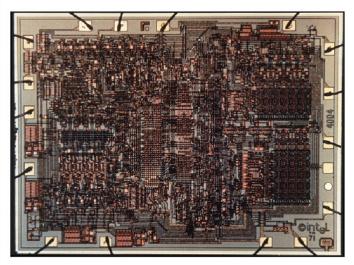


Intel 1101 256-bit SRAM Intel 4004 4-bit μProc

☐ 1980s-present: CMOS processes for low idle power

Moore's Law

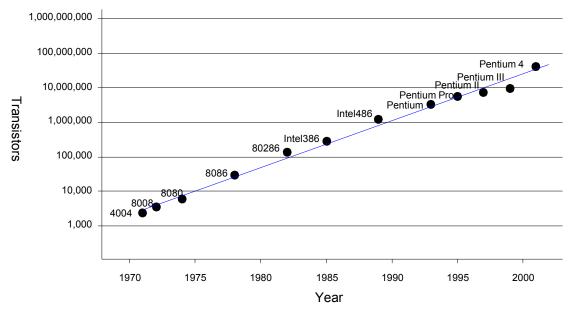- ☐ 1965: Gordon Moore plotted transistor on each chip
 - Fit straight line on semilog scale
 - Transistor counts have doubled every 26 months




Integration Levels

SSI: 10 gates


MSI: 1000 gates

LSI: 10,000 gates

VLSI: > 10k gates

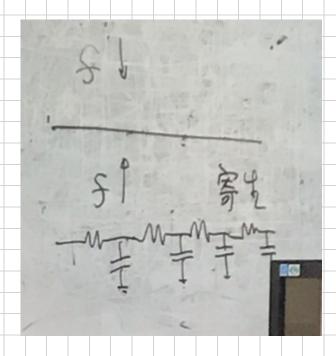

導線 在頻率高的時候 就可以看成一串 電阻 和 電容

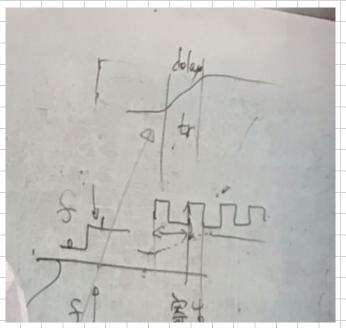


在快速電路 就會有可能 不夠 這個電壓 上升的時間

所以才會希望電路越短越好 才能越做越快

Corollaries

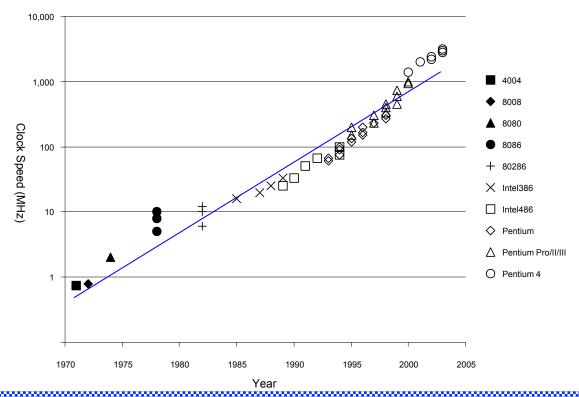
- Many other factors grow exponentially
 - Ex: clock frequency, processor performance




CMOS Gate Design

- ☐ Activity:
 - Sketch a 4-input CMOS NAND gate


NMOSFET 就簡稱叫 nMOS pMOS同理

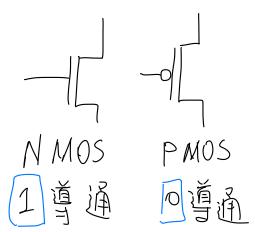


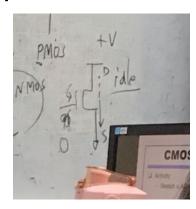

閒置的時候 也有可能有閒置電流 可能放著沒做事 也會有點熱熱的

pMOS 長得通常比較大

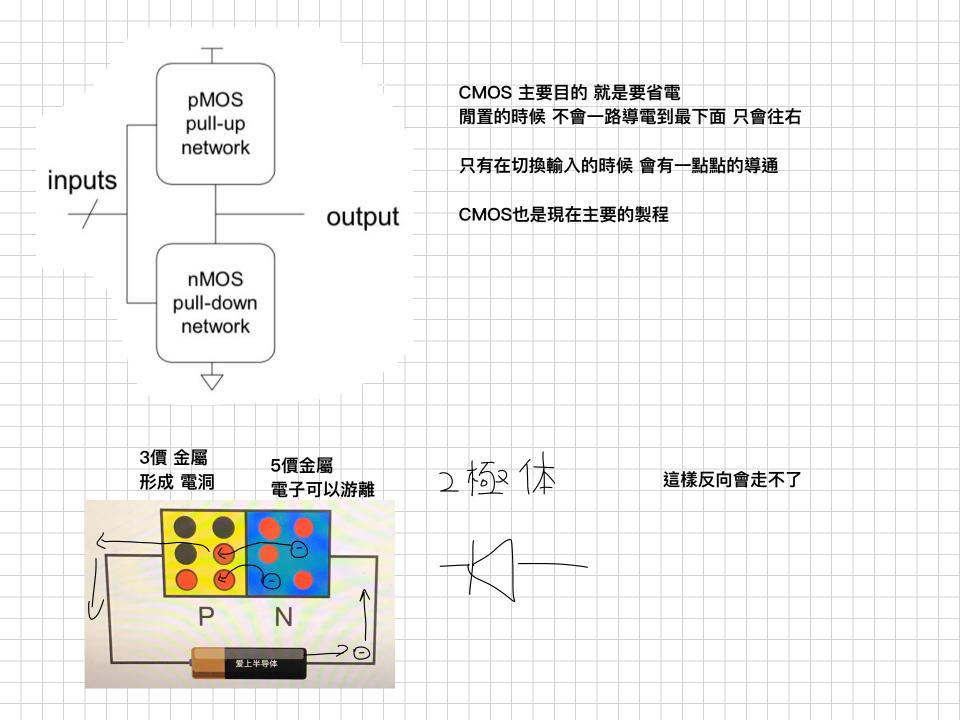

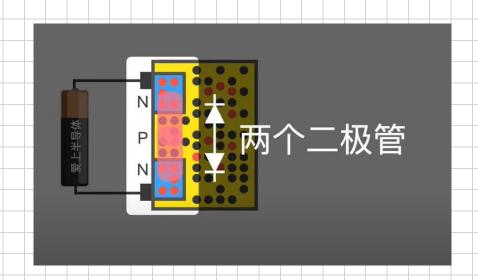


這樣原本是都不能動的

剩下自己看

https://youtu.be/HtE6inJg2XQ

https://youtu.be/5BGM9zS32F0

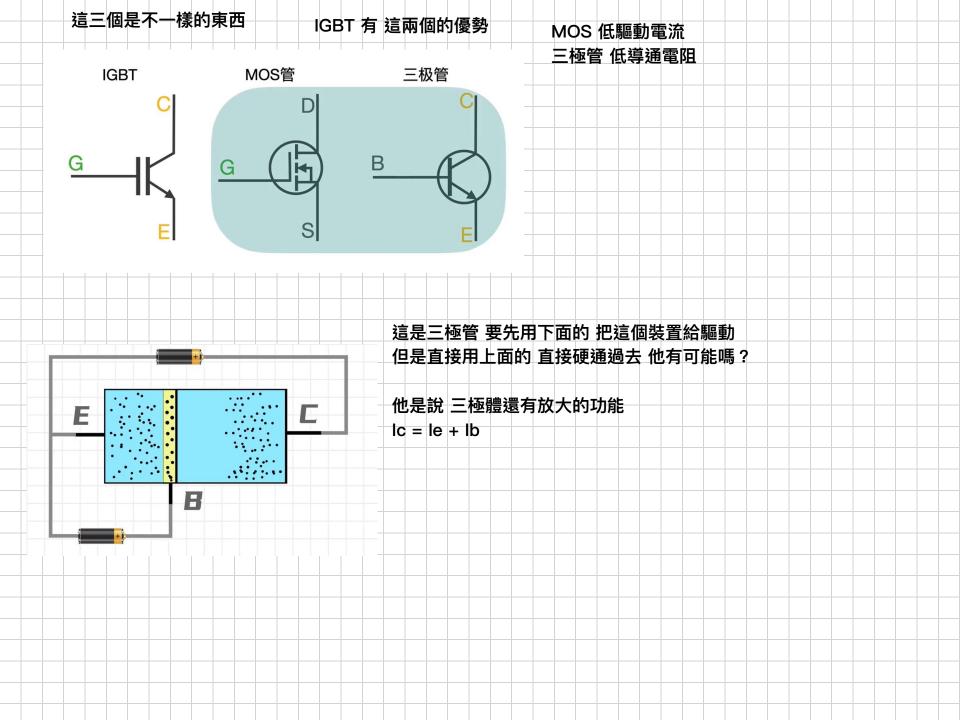




BJT 就是 這三個組在一起的名字 又叫作 三極體

https://youtu.be/sVxIYAzKjxY 這是網路上人在教的

CMOS Gate Design

□ Activity: 這個期中一定會考 給你一個邏輯閘 叫你畫出電路

Sketch a 4-input CMOS NOR gate

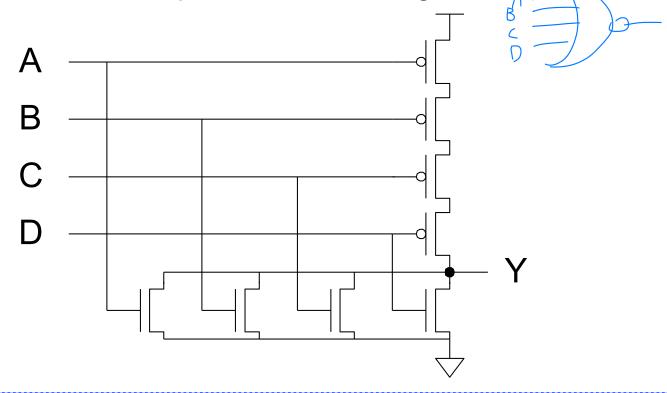

Complementary CMOS

□ Complementary CMOS logic gates

nMOS pull-down network

pMOS pull-up network

a.k.a. static CMOS

inputs pMOS pull-up network output nMOS pull-down

network

標準 pMOS 和 nMOS的分佈

兩個同時都是開的 就是壞掉的

	Pull-up OFF	Pull-up ON	
Pull-down OFF	Z (float)	1	
Pull-down ON	0	X (crowbar)	

兩個pMOS nMOS 同時都是關掉的 就是 Float 浮接 <

正常電路最好是不要有 浮接

他會向天線一樣 有頻率的整數倍 就會共振


Series and Parallel

- □ nMOS: 1 = ON
- \square pMOS: 0 = ON
- ☐ Series: both must be ON
- □ Parallel: either can be ON

		********	doccoo	
-	<i>0</i> D	DΙ	(0	1 ,
a g1— g2— b	a 0 0 b	a 0 → 1 + b	1 • 0 • b	a
(a)	OFF	OFF	OFF	ON
a g1-d g2-d b (b)	a 0 ↓ 0 ↓ b ON	a 0 ∳ 1 ob OFF	a 1 → 0 → b OFF	a 1 d 1 d b OFF
g1————————————————————————————————————	a 0 0 b	a 0 1 b	a 1 ↓ ↓ 0 b	a 1 1 1 1
(c)	OFF	ON	ON	ON
a g1⊸↓↓ ⊢ g2 b		a - 0 → 1	a 1 • 0 b	b b
(d)	ON	ON	ON	OFF

Conduction Complement

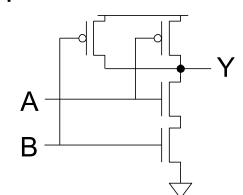- □ Complementary CMOS gates always produce 0 or 1
- □ Ex: NAND gate NAND NOR 兩個相反 電路接的方法剛好 並連串連的 pMOS nMOS剛好相反
 - Series nMOS: Y=0 when both inputs are 1
 - Thus Y=1 when either input is 0
 - Requires parallel pMOS




- ☐ Rule of Conduction Complements
 - Pull-up network is complement of pull-down
 - Parallel -> series, series -> parallel

Compound Gates


複合 邏輯閘



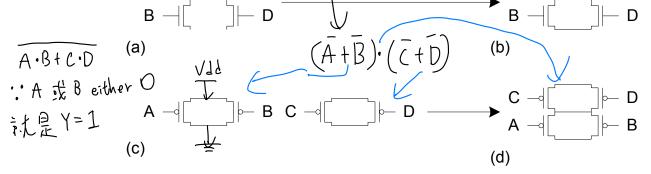
$$\square$$
 Ex: $Y = A \cdot B + C \cdot D$ (AND-AND-OR-INVERT, AOI22)



複習一下 卡諾圖 K map? 用來 精簡 電路

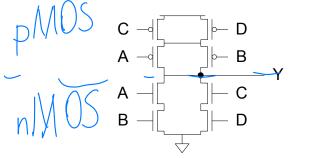


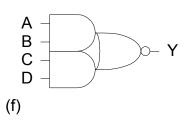

有invert pMOS 就負責處理 Y = 1 正輸出 的狀況 nMOS 就負責處理 Y = 0 負輸出 的狀況 是這樣嗎

反正通常pMOS 都畫在上面 負責和Vdd 接著 nMOS 通常都在下面 負責和 接地 接著

這pMOS nMOS 的接法 就是剛好 並連 串連 相反

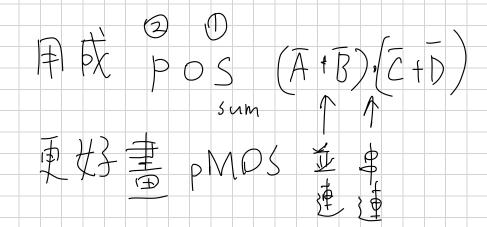

Example: 03AI

$$\square Y = \overline{(A+B+C) \cdot D}$$

Example: 03AI

$$P = (A + B + C) \cdot D$$

$$P = (A + B + C) \cdot D$$

$$P = (A + B + C) \cdot D$$


$$P = (A + B + C) \cdot D$$

Signal Strength

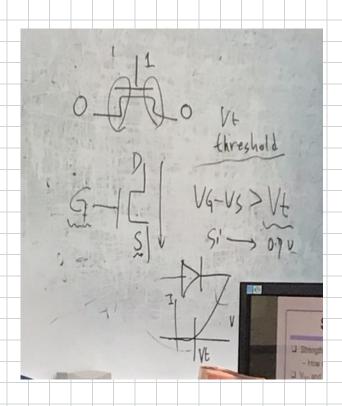
- ☐ Strength of signal
 - How close it approximates ideal voltage source
- V_{DD} and GND rails are strongest 1 and 0
- nMOS pass strong 0
 - But degraded or weak 1
- pMOS pass strong 1
 - But degraded or weak 0
- Thus nMOS are best for pull-down network



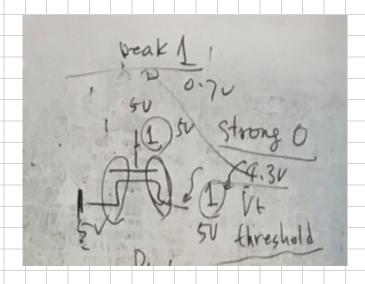這個nMOS 要能夠導通 也要必須大於 threshold Vt nMOS 可以讓 0 完整的通過 叫做 strong 0



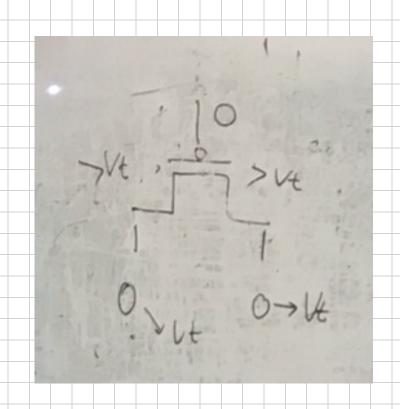上面這個5V 就像是要幫下面要通過的地方 拉開一個 通道 他必須要拉超過 Vt的高度 左邊的電流 才有可能可以留過去 但是留過去的最大量 不會超過 5V - 0.7 =4.3V 所以才會叫做 weak 1



pMOS 0導通 比較奇特一點 他要通過也需要超過Vt 也就導致 0要通過 也會被拉高成 到Vt的強度 但他是strong 1 不太懂

所以 pMOS 才會通常用來負責 Y = 1 nMOS 才會通常用來負責 Y = 0

Pass Transistors

☐ Transistors can be used as switches

Pass Transistors

☐ Transistors can be used as switches

$$g = 0$$
$$s - - d$$

$$g = 1$$

 $s \rightarrow d$

$$g = 0$$

 $s \rightarrow d$

$$g = 1$$
 $s \rightarrow \phi \rightarrow d$

Input
$$g = 1$$
 Output $0 \rightarrow strong 0$


Input
$$g = 0$$
 Output $0 \rightarrow -$ degraded 0


Transmission Gates

- Pass transistors produce degraded outputs
- ☐ Transmission gates pass both 0 and 1 well

但是他這樣 要串連 就有可能一直要減 Vt

所以就會把它弄成這樣子 並連 讓訊號不要衰減

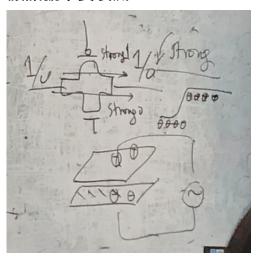

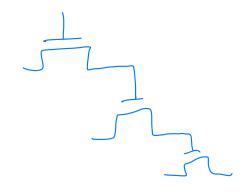

這是一個電容?

但弄成這樣 雜訊也會很容易通過

Transmission Gates

- Pass transistors produce degraded outputs
- ☐ Transmission gates pass both 0 and 1 well

$$g = 0$$
, $gb = 1$
 $a - b$

$$g = 1$$
, $gb = 0$
 $a \rightarrow b$

Input Output

$$g = 1$$
, $gb = 0$
 $0 \rightarrow \rightarrow c$ strong 0

$$g = 1$$
, $gb = 0$
 $1 \rightarrow \infty$ strong 1

Tristates


這是一個 緩衝器 不然電線也會消耗一些 就是中繼器

☐ Tristate buffer produces Z when not enabled

EN	Α	Υ
0	0	2
0	1	区
1	0	
1	1	

高阻態

High enbedays

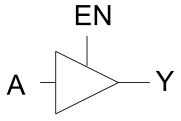


Tristates

☐ *Tristate buffer* produces Z when not enabled

EN	А	Υ
0	0	Z
0	1	Z
1	0	0
1	1	1


Nonrestoring Tristate

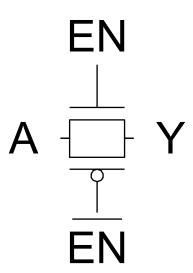- ☐ Transmission gate acts as tristate buffer
 - Only two transistors
 - But nonrestoring 没有辦法
 - Noise on A is passed on to Y




Tristate Inverter

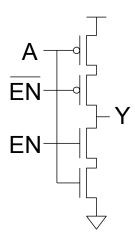- ☐ Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Tristate Inverter

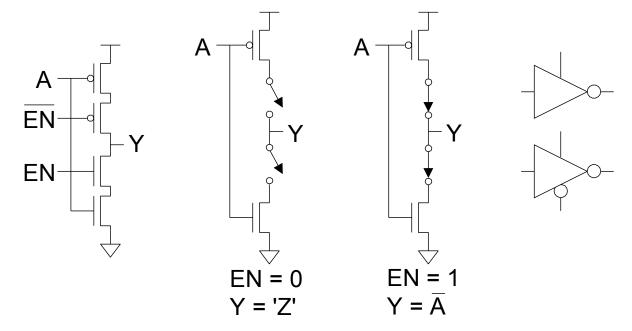
- ☐ Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Multiplexers

☐ 2:1 *multiplexer* chooses between two inputs


S	D1	D0	Υ
0	X	0	
0	X	1	
1	0	X	
1	1	X	

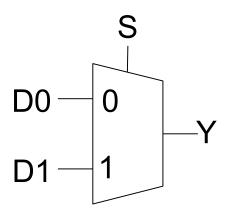

Multiplexers

☐ 2:1 multiplexer chooses between two inputs

S	D1	D0	Υ
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

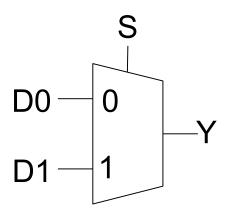


Gate-Level Mux Design

- \square $Y = SD_1 + SD_0$ (too many transistors)
- ☐ How many transistors are needed?


Gate-Level Mux Design

- \Box $Y = SD_1 + SD_0$ (too many transistors)
- ☐ How many transistors are needed? 20


這樣會需要太多電晶體

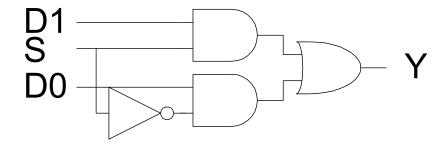



但不知道為什麼要加這麼多not

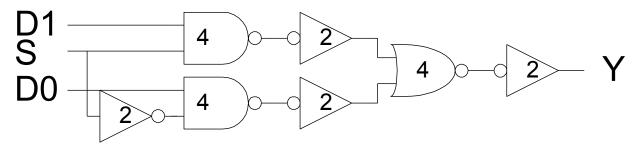


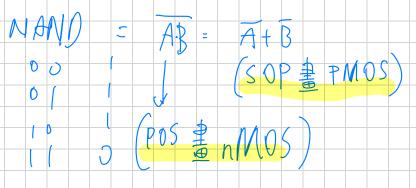
因為要組成邏輯閘 就是要用這些電路組成 這些電路 組成nand nor 更方便 要組成and 就是要再加上 not




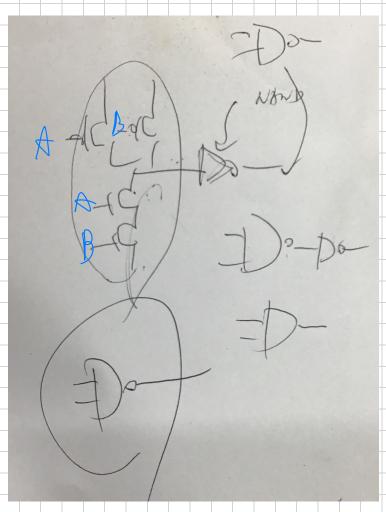

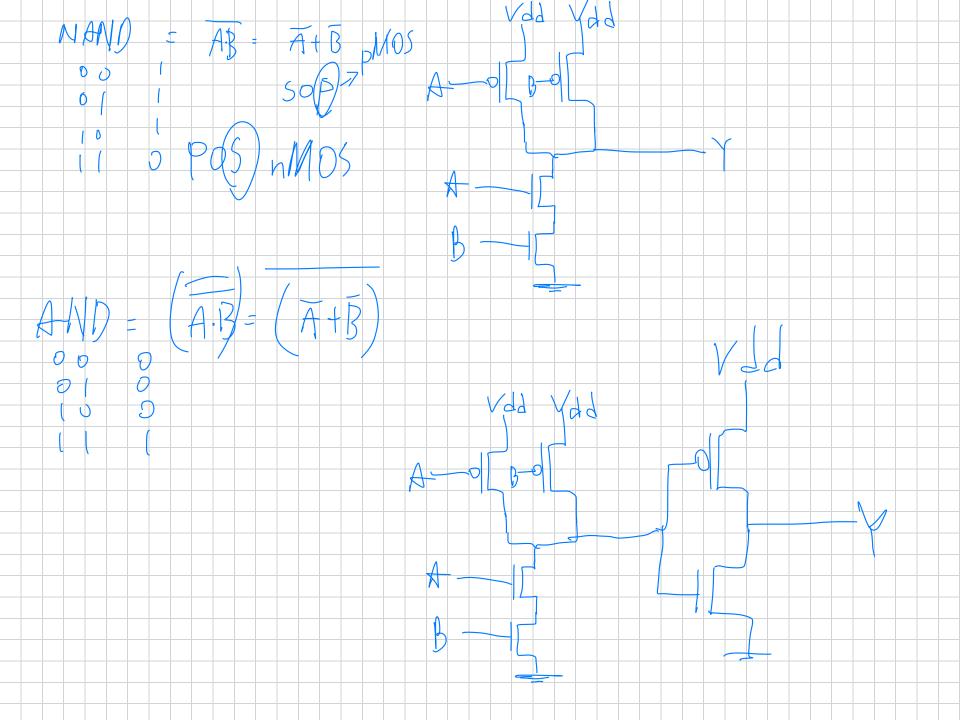

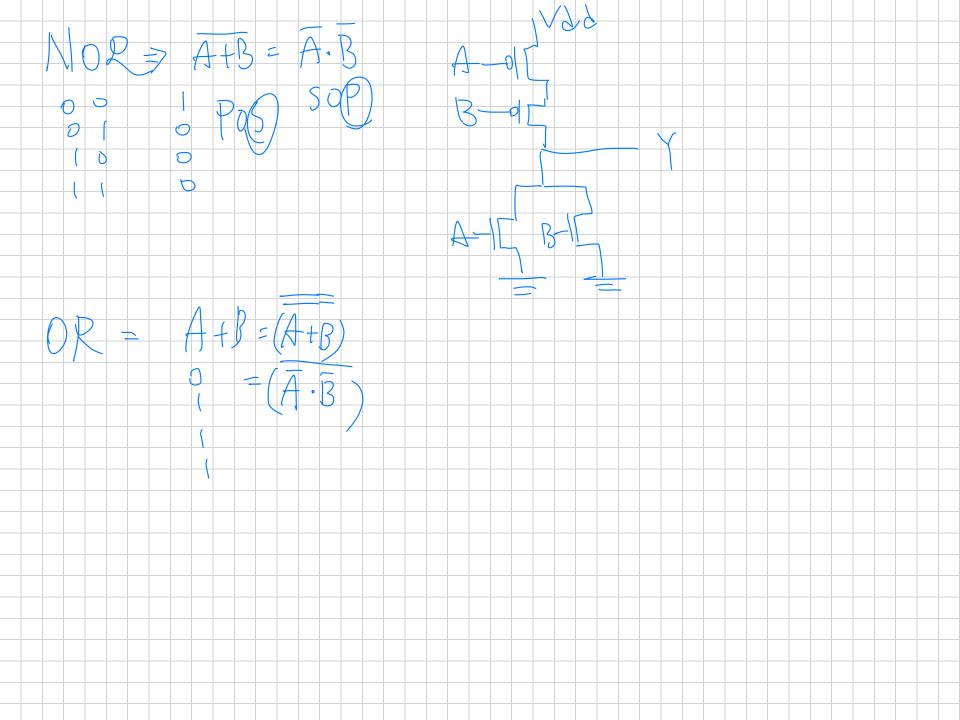

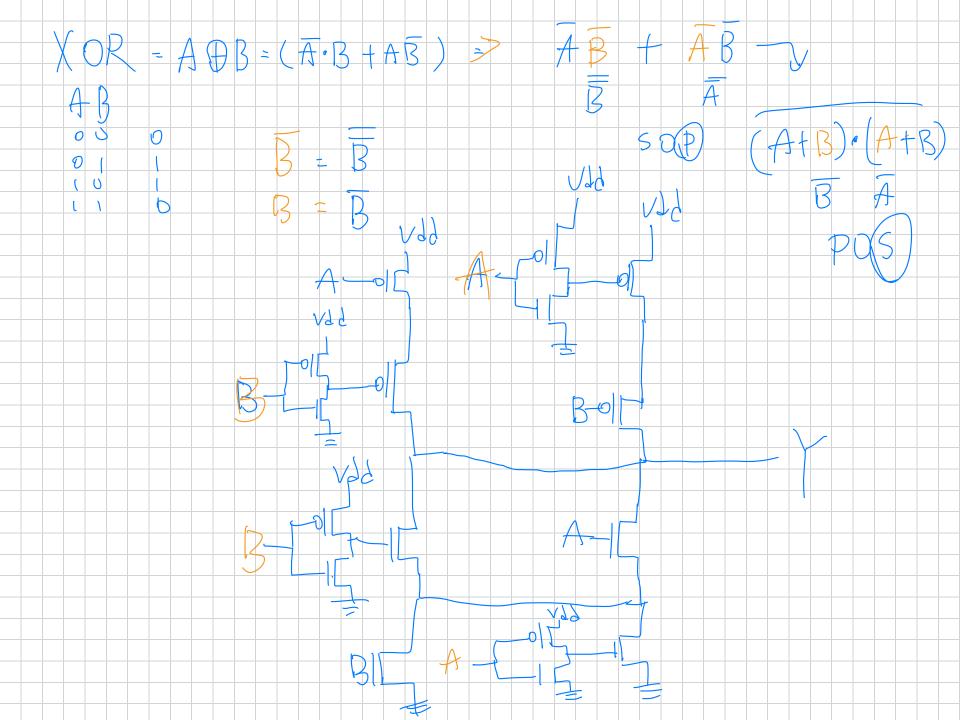

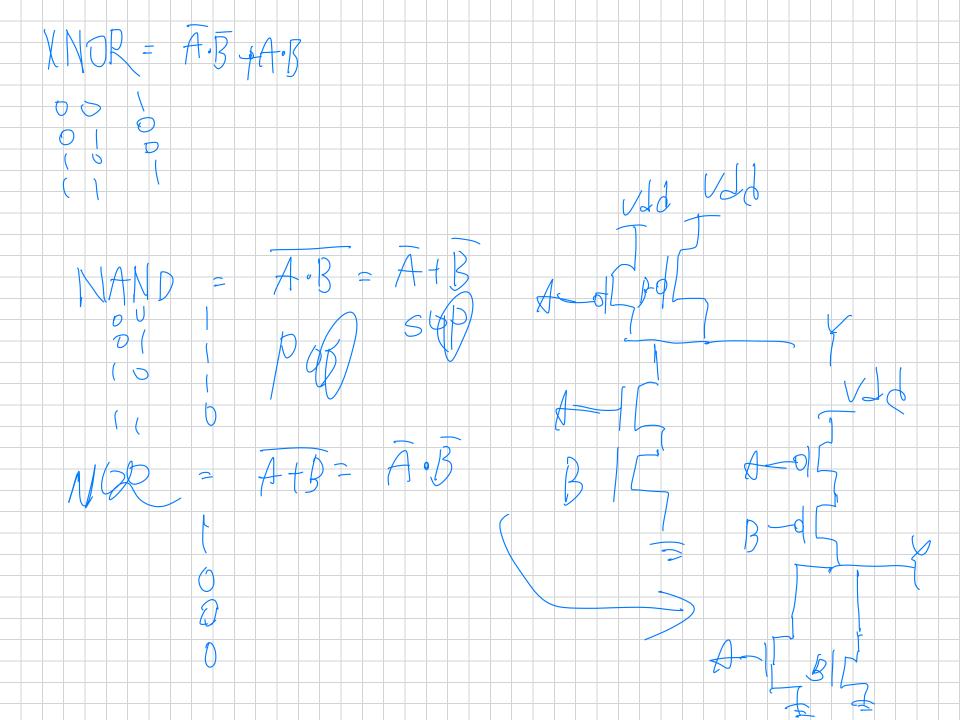


Transmission Gate Mux

■ Nonrestoring mux uses two transmission gates


Transmission Gate Mux

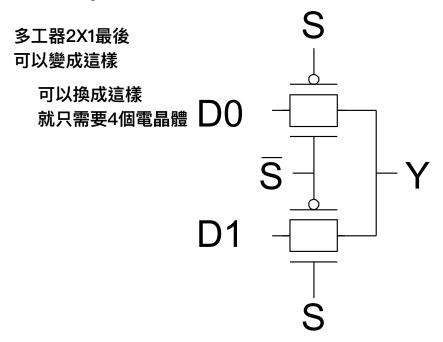
- Nonrestoring mux uses two transmission gates
 - Only 4 transistors




Inverting Mux

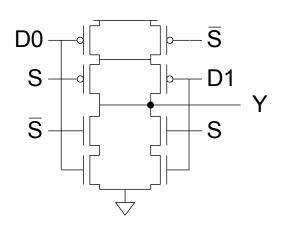- □ Inverting multiplexer
 - Use compound AOI22
 - Or pair of tristate inverters
 - Essentially the same thing
- Noninverting multiplexer adds an inverter



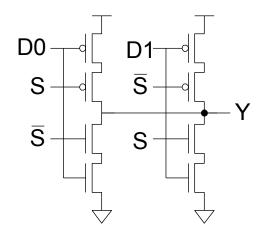

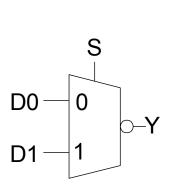



4:1 Multiplexer

☐ 4:1 mux chooses one of 4 inputs using two selects

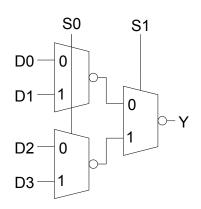4:1 Multiplexer


- ☐ 4:1 mux chooses one of 4 inputs using two selects
 - Two levels of 2:1 muxes
 - Or four tristates



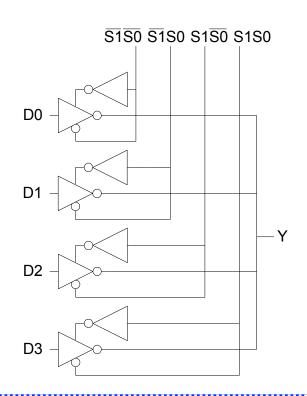


D Latch

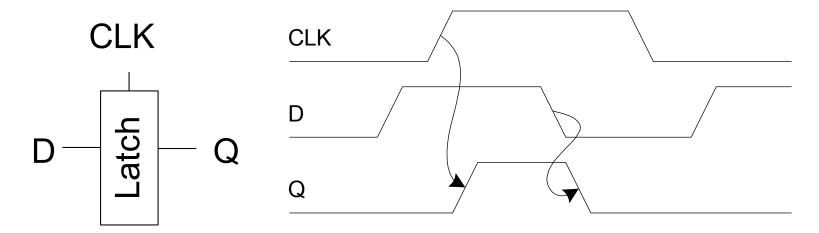- ☐ When CLK = 1, latch is *transparent*
 - D flows through to Q like a buffer
- When CLK = 0, the latch is opaque
 - Q holds its old value independent of D
- ☐ a.k.a. transparent latch or level-sensitive latch




D Latch Design

■ Multiplexer chooses D or old Q

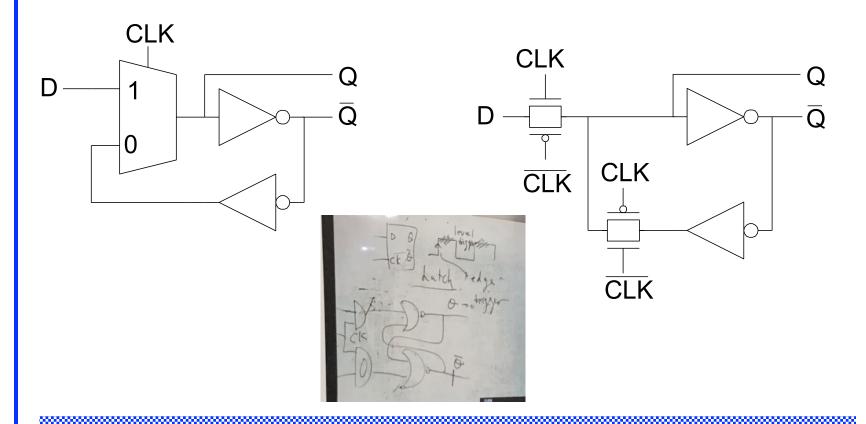

> Level trigger


D Latch Operation

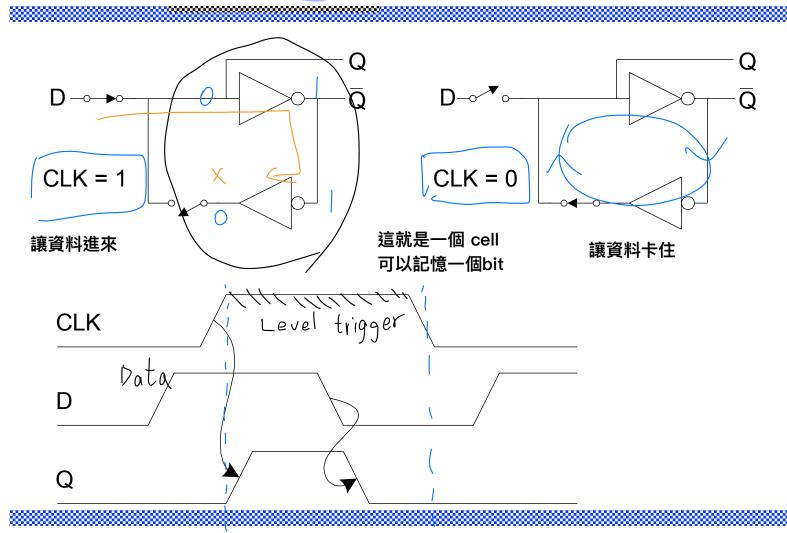


— edge trigger

D Flip-flop

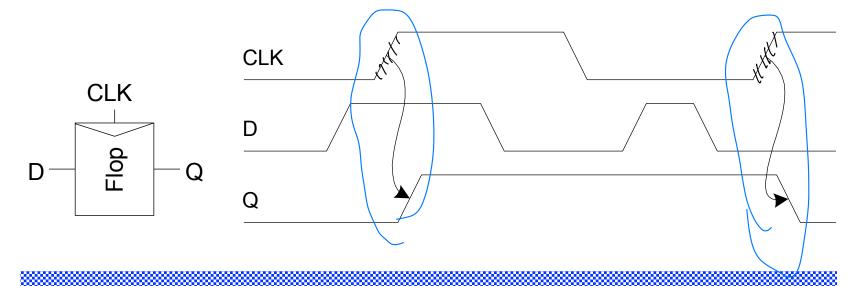- When CLK rises, D is copied to Q
- ☐ At all other times, Q holds its value
- □ a.k.a positive edge-triggered flip-flop, master-slave flip-flop 正觸發




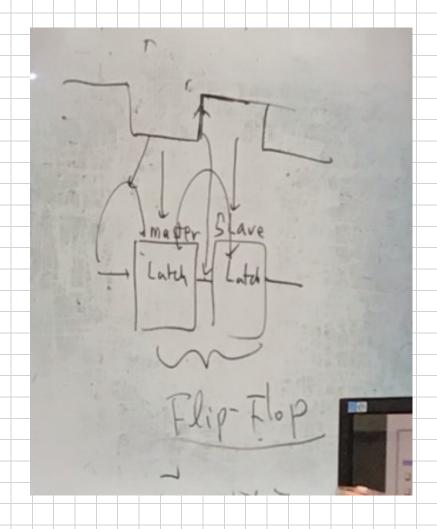


Flip Flop 是用兩個Latch 鬥出來的 主僕式 正反器

D Flip-flop Design

■ Built from master and slave D latches

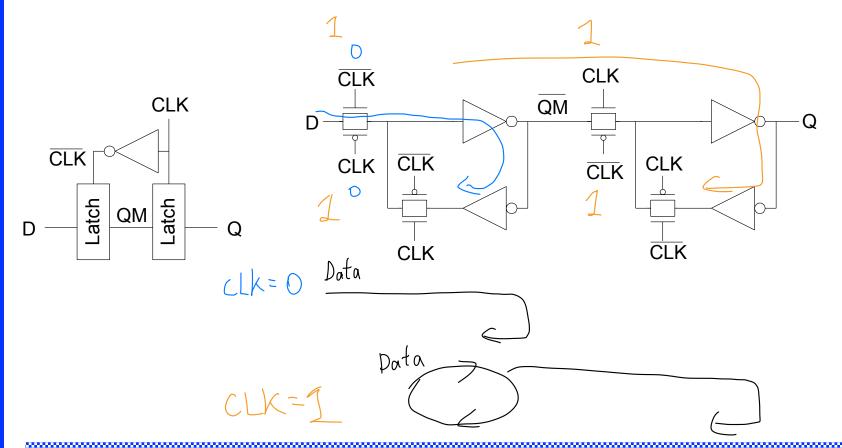



D Flip-flop Operation

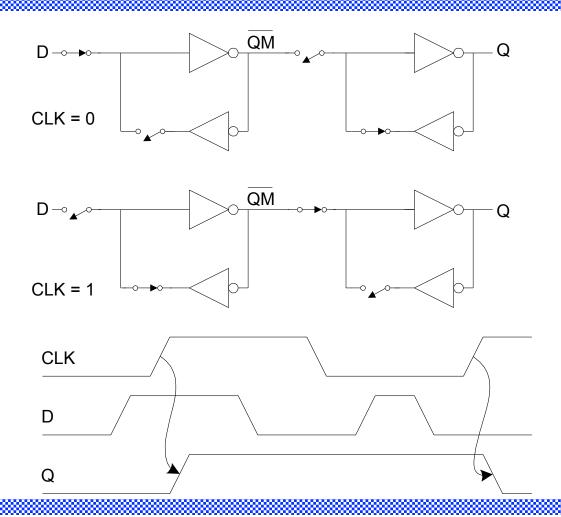


Race Condition

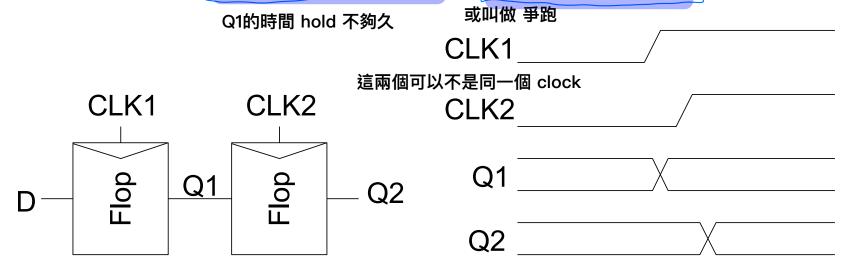- Back-to-back flops can malfunction from clock skew
 - Second flip-flop fires late 可能會提前把中間的資料提前蓋掉了
 - Sees first flip-flop change and captures its result
 - Called hold-time failure or race condition



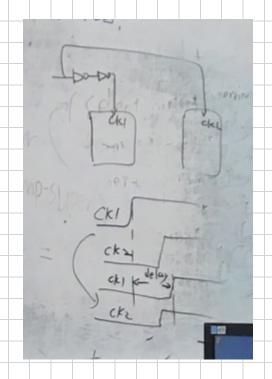

也有一種方法 是用兩個not的延遲 來解決 爭跑問題

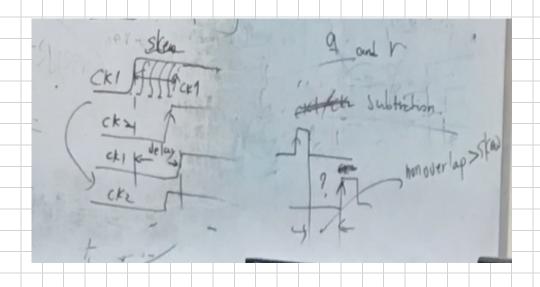


可能元件老化 就有可能造成 偏易skew的clock

所以希望資料傳輸間 的 間距時間 Nonoverlap > skew

Nonoverlapping Clocks

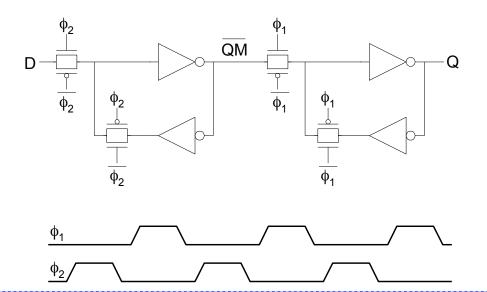- Nonoverlapping clocks can prevent races
 - As long as nonoverlap exceeds clock skew
- We will use them in this class for safe design
 - Industry manages skew more carefully instead



Gate Layout

- Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells

- ☐ Standard cell design methodology
 - V_{DD} and GND should abut (standard height)
 - Adjacent gates should satisfy design rules
 - nMOS at bottom and pMOS at top
 - All gates include well and substrate contacts

nMOS pMOS 之間就是 迪摩 根定理的轉換

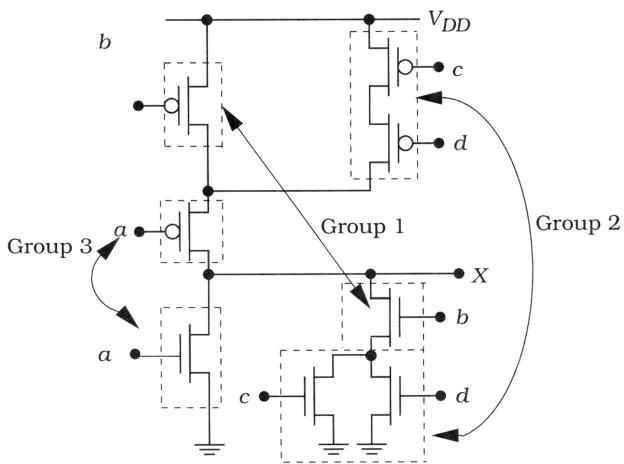
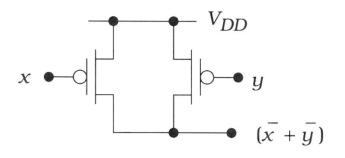
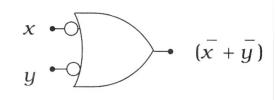


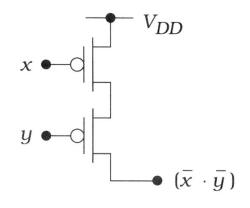



Figure 2.49 AOI circuit for Example 2.1





(a) Parallel-connected pFETs



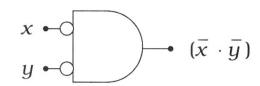

(b) Series-connected pFETs

Figure 2.51 Assert-low models for pFETs

1: Circuits &

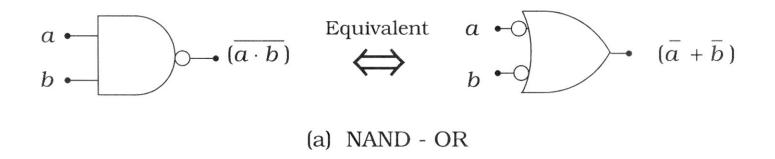


Figure 2.52 Bubble pushing using DeMorgan rules



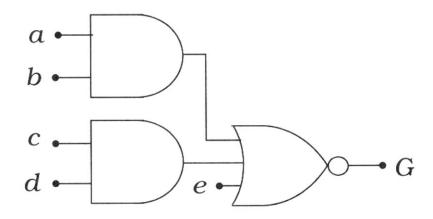


Figure 2.53 AOI logic diagram for bubble-pushing example

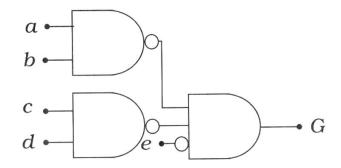

(a) First transformation

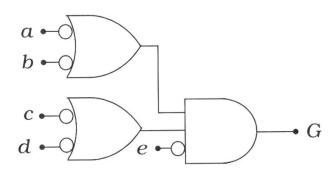

(b) Final form

Figure 2.54 Bubble pushing to obtain the topology of the pFET array

1: Circ

de 50

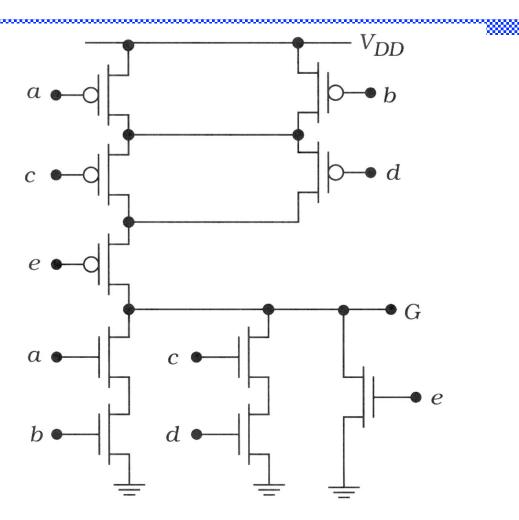



Figure 2.55 Final circuit for the bubble-pushing example


1: Circuits ∝ ∟ayout

CIVICO VLOI DESIGII

Slide 51


Example: Inverter

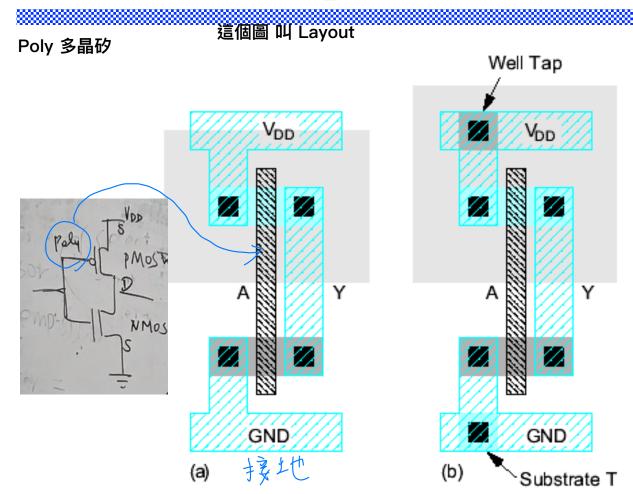

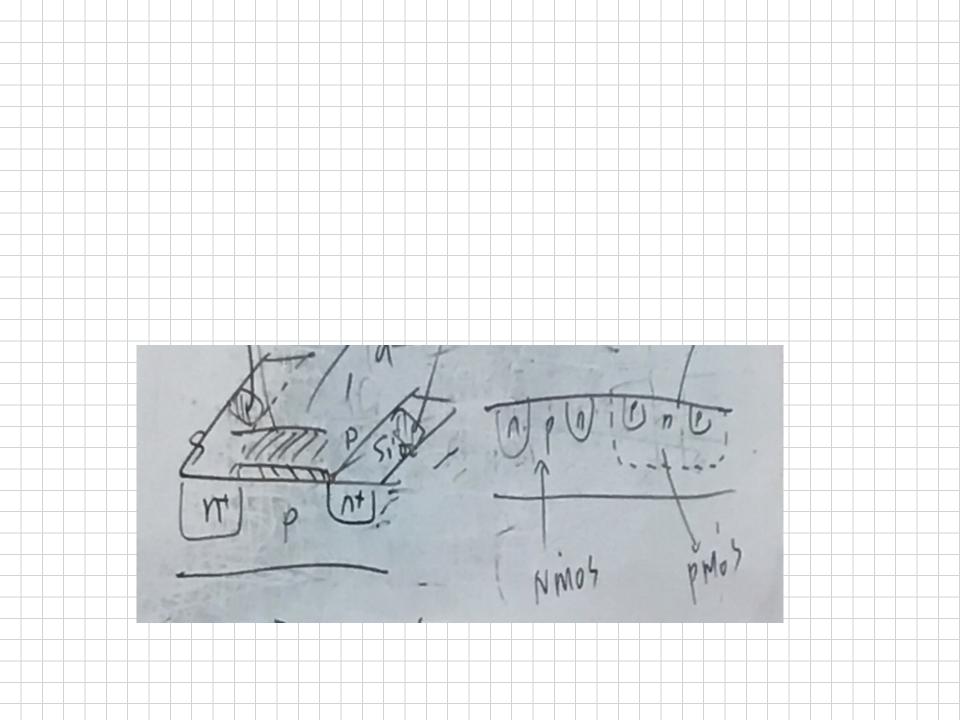

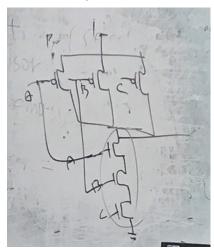
Example: NAND3

- ☐ Horizontal N-diffusion and p-diffusion strips
- □ Vertical polysilicon gates
- Metal1 V_{DD} rail at top
- Metal1 GND rail at bottom
- \Box 32 λ by 40 λ




黑色正方形 就是要接出來 走電線的地方


淡藍色斜線 就是電線

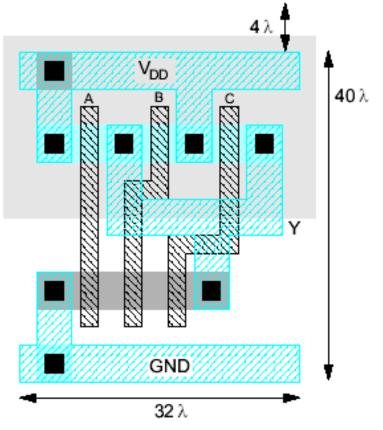


Stick Diagrams

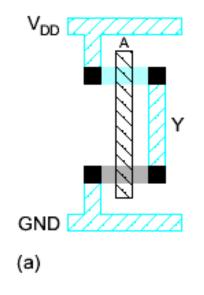- ☐ Stick diagrams help plan layout quickly
 - Need not be to scale
 - Draw with color pencils or dry-erase markers




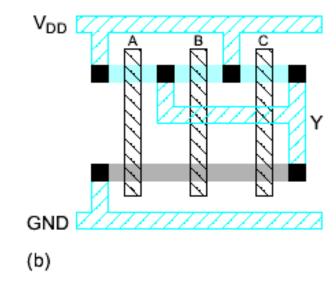

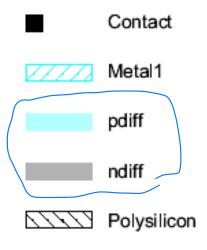


Wiring Tracks

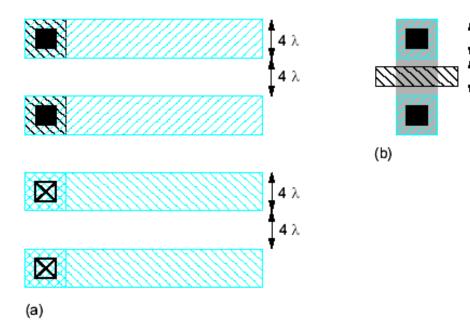- ☐ A wiring track is the space required for a wire
 - -4λ width, 4λ spacing from neighbor = 8λ pitch
- ☐ Transistors also consume one wiring track




Well spacing

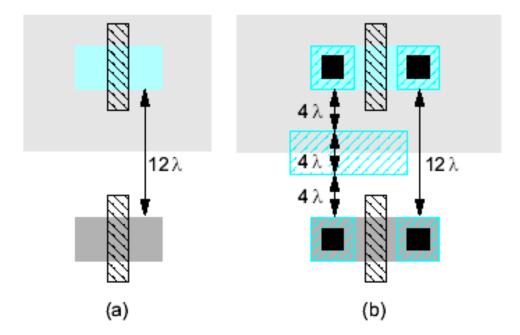- \Box Wells must surround transistors by 6 λ
 - Implies 12 λ between opposite transistor flavors
 - Leaves room for one wire track



Area Estimation

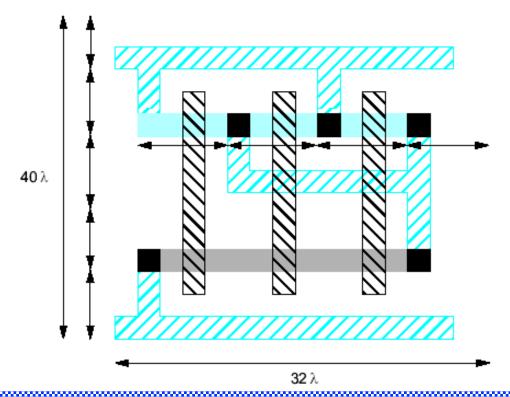- ☐ Estimate area by counting wiring tracks
 - Multiply by 8 to express in λ



1: Circuits & Layout


Example: O3AI

Sketch a stick diagram for O3AI and estimate area $Y = (A + B + C) \cdot D$

Example: O3AI

☐ Sketch a stick diagram for O3AI and estimate area

$$- Y = (A + B + C) \cdot D$$

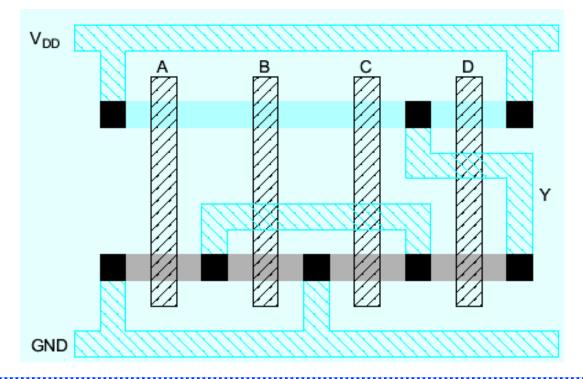

Example: O3AI

☐ Sketch a stick diagram for O3AI and estimate area

$$- Y = \overline{(A+B+C) \cdot D}$$

