

# **Introduction to CMOS VLSI Design**

## **Lecture 5: Logical Effort**


# Outline

---

- ☐ Introduction
- ☐ Delay in a Logic Gate
- ☐ Multistage Logic Networks
- ☐ Choosing the Best Number of Stages
- ☐ Example
- ☐ Summary
 
# Introduction

- ❑ Chip designers face a bewildering array of choices
  - What is the best circuit topology for a function?
  - How many stages of logic give least delay?
  - How wide should the transistors be?
- ❑ Logical effort is a method to make these decisions
  - Uses a simple model of delay
  - Allows back-of-the-envelope calculations
  - Helps make rapid comparisons between alternatives
  - Emphasizes remarkable symmetries



# Example


- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- ❑ Decoder specifications:


- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs  $A[3:0]$
- Each input may drive 10 unit-sized transistors

- ❑ Ben needs to decide:

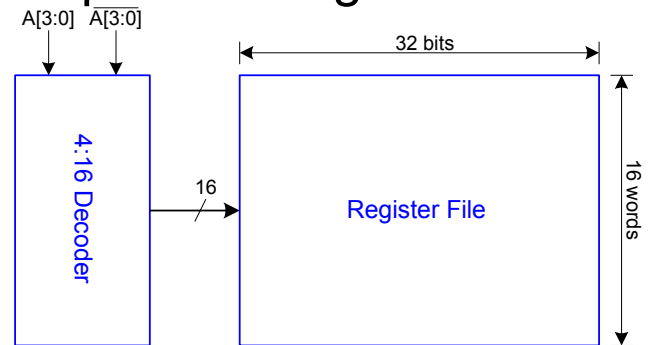- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



這是一個  $2 \times 4$  的decoder

 

# Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$$\tau = 3RC \quad \text{延遲參數}$$

$\approx$  12 ps in 180 nm process

40 ps in 0.6  $\mu\text{m}$  process

# Delay in a Logic Gate

- ❑ Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

寄生電容

# Delay in a Logic Gate

- ❑ Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

- ❑ *Effort delay*  $f = gh$  (a.k.a. *stage effort*)
  - Again has two components



# Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

g 和邏輯夾 的種類有關

- Effort delay  $f = gh$  (a.k.a. stage effort)

- Again has two components

- $g$ : *logical effort*

- Measures relative ability of gate to deliver current
- $g \equiv 1$  for inverter

# Delay in a Logic Gate

- ❑ Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$


- ❑ Effort delay  $f = gh$  (a.k.a. stage effort)

- Again has two components

- ❑  $h$ : electrical effort =  $C_{out} / C_{in}$

- Ratio of output to input capacitance

- Sometimes called fanout

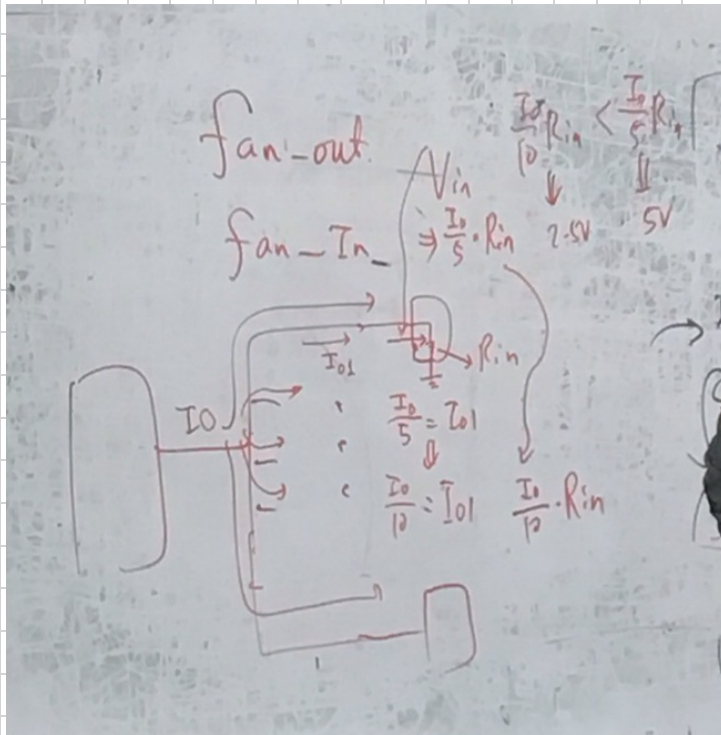

可能會因為 接的電路多了  
電壓就被分散了 就叫fanout

Fan in 和接地的分散有關

# Delay in a Logic Gate

- ❑ Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

這裡要講p


- ❑ Parasitic delay  $p$ 
  - Represents delay of gate driving no load
  - Set by internal parasitic capacitance

由 寄生電容 來定的

# Delay Plots

$$d = f + p$$
$$= gh + p$$

這裡的線從這公式得到的


 



# Delay Plots

$$d = f + p$$

$$= gh + p$$

□ What about NOR2?

  

 



$$g = \frac{4}{3}$$

$$D = \frac{4}{3} \cdot 1 + 2$$
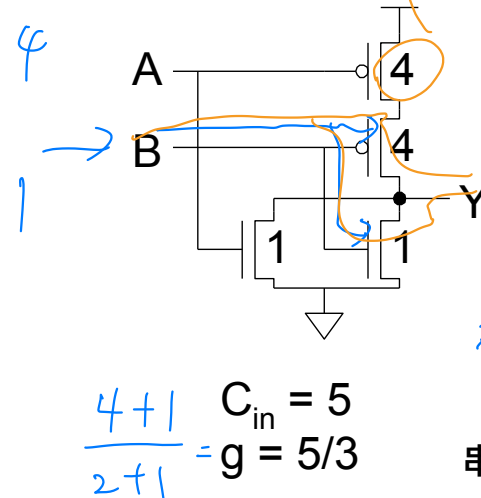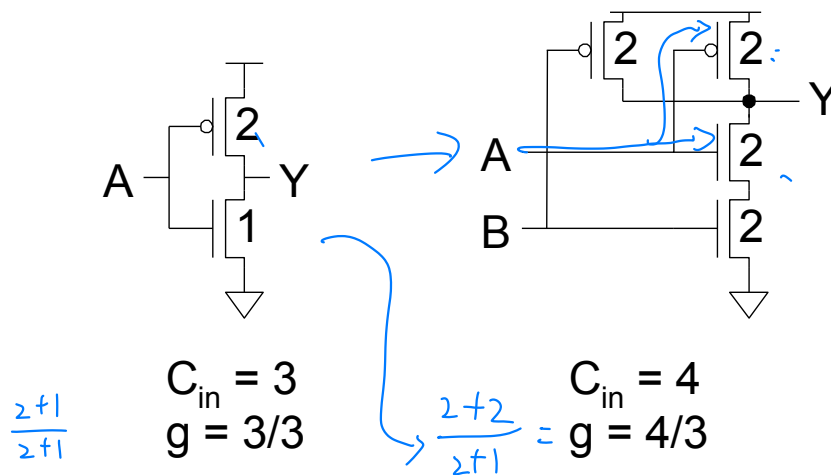
# Computing Logical Effort

- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*

- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths






Handwritten notes in Chinese:

- 希望 and not 等效 (Equivalent to hope and not)
- $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$
- $\frac{1}{2} = \frac{1}{4} + \frac{1}{4}$
- 好像不是 (Seems not)
- 好像是 (Seems to be)
- 和 W 宽度相關 (Related to W width)

串連幾個 放大幾倍 (Connect several, amplify several times)



寄生電容  
並聯的都要算  
串連的只算一個

   



# Catalog of Gates

## □ Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

# Catalog of Gates

## □ Parasitic delay of common gates


– In multiples of  $p_{inv}$  ( $\approx 1$ )

要全算

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	
 
# Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort:  $g =$

Electrical Effort:  $h =$


Parasitic Delay:  $p =$

Stage Delay:  $d =$

Frequency:  $f_{\text{osc}} =$
 
# Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort:  $g = 1$



Electrical Effort:  $h = 1$

Parasitic Delay:  $p = 1$

Stage Delay:  $d = 2$


Frequency:  $f_{\text{osc}} = 1/(2 \cdot N \cdot d) = 1/4N$

  31 stage ring oscillator in  
0.6  $\mu\text{m}$  process has  
frequency of  $\sim 200$  MHz



$$\frac{C_{out}}{C_{in}} = \frac{3}{3} = 1 = h$$


$$C_{out} = 2 + 1 = 3$$

 

$$f = \frac{1}{T} = \frac{1}{2d \cdot N}$$
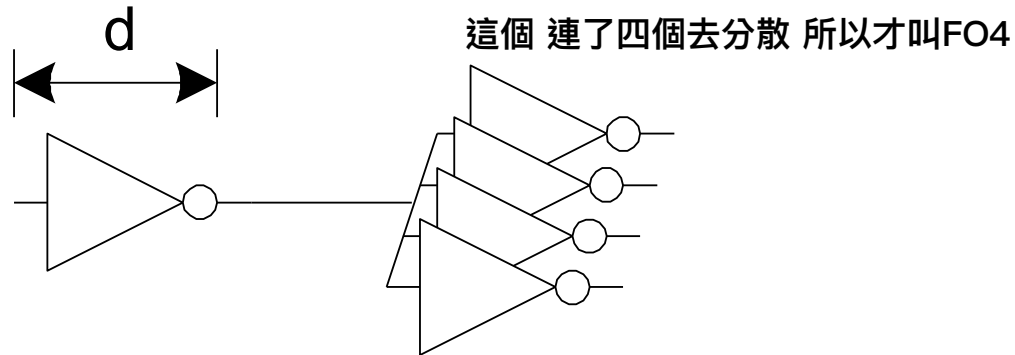
# Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g =$

Electrical Effort:  $h =$


Parasitic Delay:  $p =$

Stage Delay:  $d =$


 
# Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g = 1$

Electrical Effort:  $h = 4$

Parasitic Delay:  $p = 1$

Stage Delay:  $d = 5$

$$d = g h + p$$

The FO4 delay is about

200 ps in 0.6  $\mu\text{m}$  process

60 ps in a 180 nm process

$f/3$  ns in an  $f$   $\mu\text{m}$  process

# Multistage Logic Networks

❑ Logical effort generalizes to multistage networks


❑ *Path Logical Effort*  $G = \prod g_i$

❑ *Path Electrical Effort*  $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

❑ *Path Effort*

$$F = \prod f_i = \prod g_i h_i$$

相乘起來

 

h. h. h. h. h.

$$\Rightarrow \frac{20}{\cancel{2}} \cdot \frac{\cancel{2}}{4} \cdot \frac{\cancel{X}}{\cancel{*}} \cdot \frac{*}{10}$$

$$h = \frac{20}{10}$$

# Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort*  $G = \prod g_i$

❑ *Path Electrical Effort*  $H = \frac{C_{out-path}}{C_{in-path}}$

❑ *Path Effort*  $F = \prod f_i = \prod g_i h_i$

❑ Can we write  $F = GH$ ?

不可這樣算

# Paths that Branch

❑ No! Consider paths that branch:

$G =$


$H =$

$GH =$

$h_1 =$

$h_2 =$

$F = GH?$

 

# Paths that Branch

❑ No! Consider paths that branch:

$$H = \frac{C_{out}}{C_{in}}$$

$$G = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$


$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

 



# Branching Effort

- ❑ Introduce *branching effort*
  - Accounts for branching between stages in path


$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- ❑ Now we compute the path effort
  - $F = GBH$

# Multistage Delays

- ❑ Path Effort Delay  $D_F = \sum f_i$
- ❑ Path Parasitic Delay  $P = \sum p_i$
- ❑ Path Delay  $D = \sum d_i = D_F + P$



# Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort


$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
  - Find fastest possible delay
  - Doesn't require calculating gate sizes

$$F: A \rightsquigarrow B$$

 

$$\begin{aligned} F &= S_A \cdot f_A \cdot f_C \cdot \frac{1}{3} \\ &= \hat{f} \quad \hat{f} = F \end{aligned}$$

# Gate Sizes

- How wide should the gates be for least delay?

$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$


$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.


# Example: 3-stage path

- Select gate sizes  $x$  and  $y$  for least delay from  $A$  to  $B$

要得到最小的延遲 從a到b  $x$ 和 $y$ 要多大

 

# Example: 3-stage path

 

Logical Effort  $G =$

Electrical Effort  $H =$

Branching Effort  $B =$


Path Effort  $F =$

Best Stage Effort  $\hat{f} =$

Parasitic Delay  $P =$

Delay  $D =$

# Example: 3-stage path

 

Logical Effort

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

Electrical Effort

$$H = 45/8$$

Branching Effort

$$B = 3 * 2 = 6$$

Path Effort

$$F = GBH = 125$$

Best Stage Effort

$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic Delay

$$P = 2 + 3 + 2 = 7$$

Delay


$$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$$

# Example: 3-stage path

- Work backward for sizes

$y =$

$x =$

 


## Example: 3-stage path

- ❑ Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$


$$x = (15 * 2) * (5 / 3) / 5 = 10$$

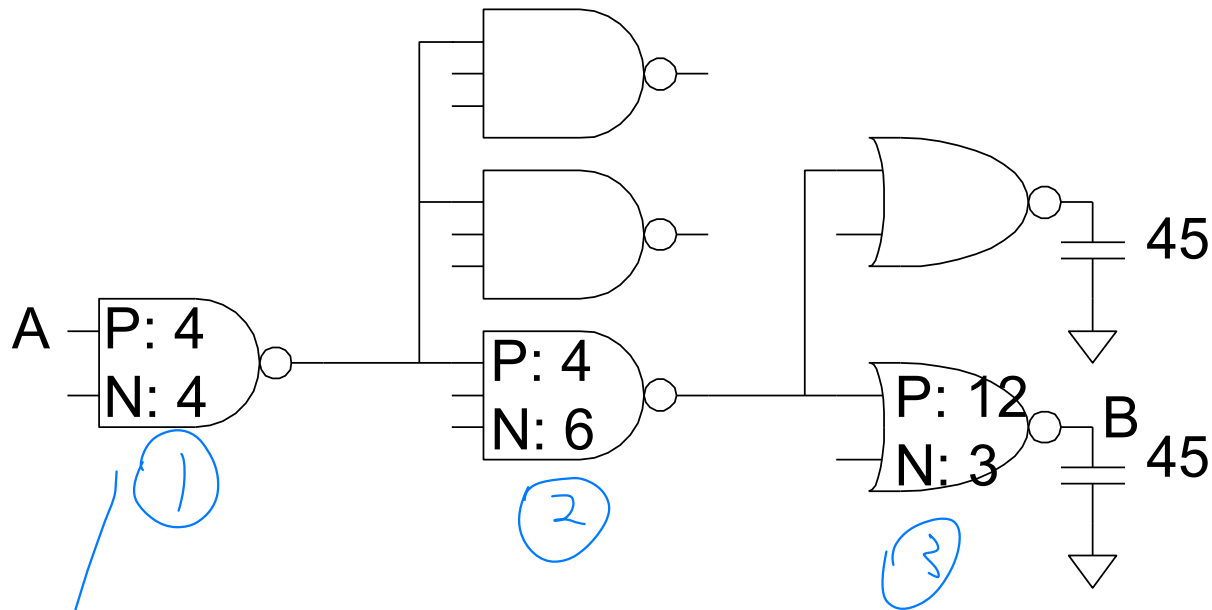



$$\hat{f} = gh$$
 
$$f(12) = g \frac{C_{out}}{C_{in}} \Rightarrow C_{in} = \frac{g \cdot C_{out}}{f} \quad \hat{f} = F^{\frac{1}{n}}$$



4pF

15pF

$$C_{in} = \frac{5 \cdot 45}{5} = 15$$


$$15 \cdot \frac{4}{4+1} = 12$$


$$15 \cdot \frac{4}{4+1} = 12$$

$$15 \cdot \frac{1}{4+1} = 3$$

win

(2)

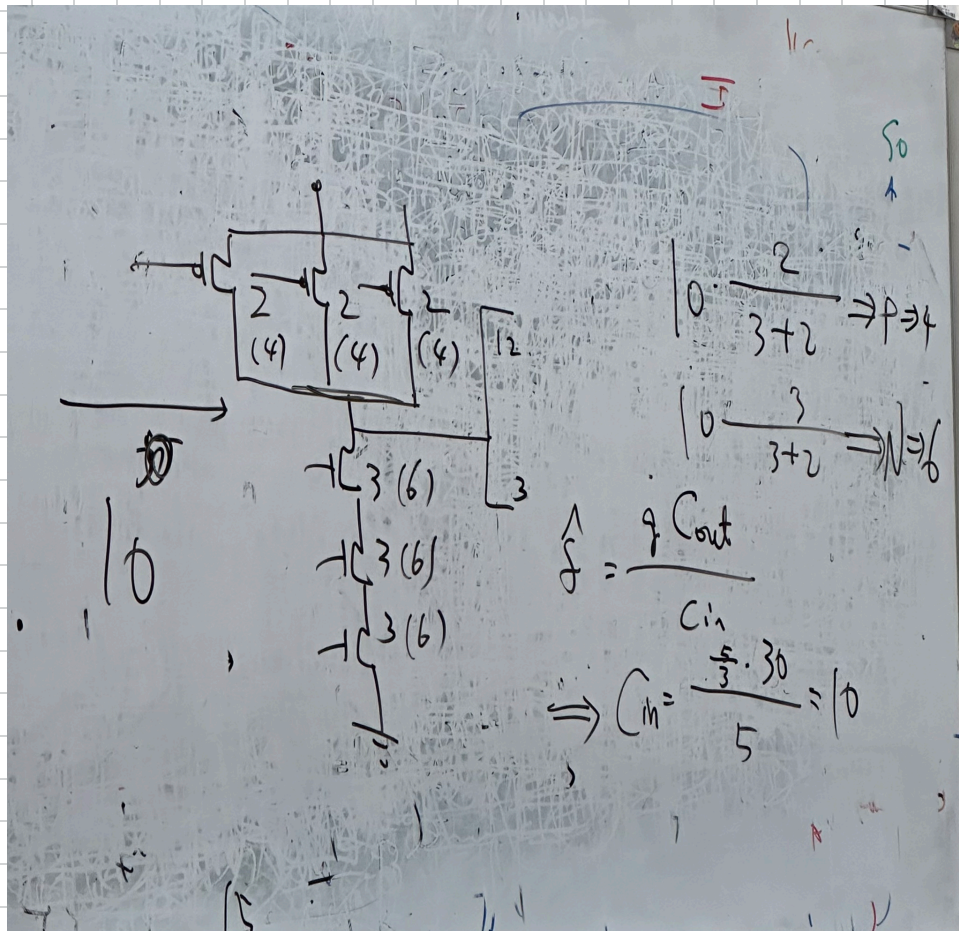

 

$$8 \cdot \frac{2}{2+2} = 4(P)$$

$$7 \cdot \frac{2}{2+2} = 4(N)$$

$$C_{in} = \frac{\frac{4}{3} \cdot 30}{5} = 8$$

$$f = \frac{g C_{out}}{C_{in}} \Rightarrow C_m = \frac{\frac{5}{3} \cdot 30}{5} = 10$$


$$10 \cdot \frac{2}{3+2} \Rightarrow P \Rightarrow 4$$

$$10 \cdot \frac{3}{3+2} \Rightarrow N \Rightarrow 6$$

# Best Number of Stages

- ❑ How many stages should a path use?
  - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter

D =

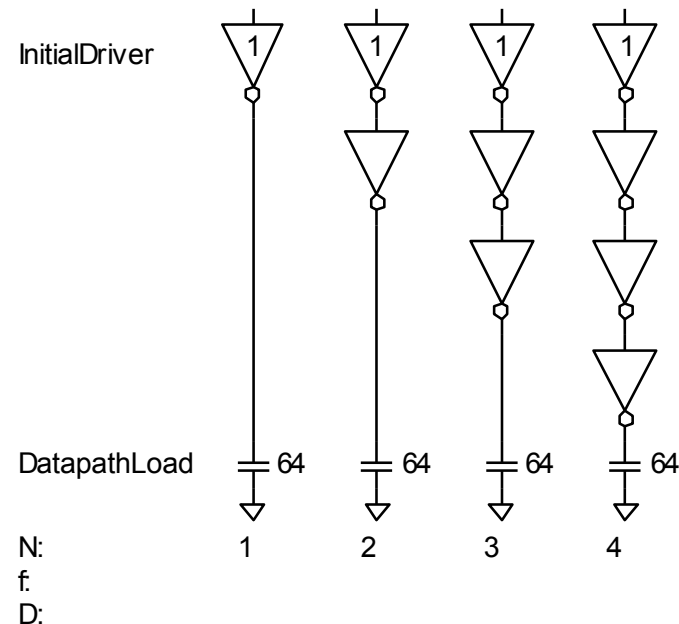


# Best Number of Stages

- ❑ How many stages should a path use?
  - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter


$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

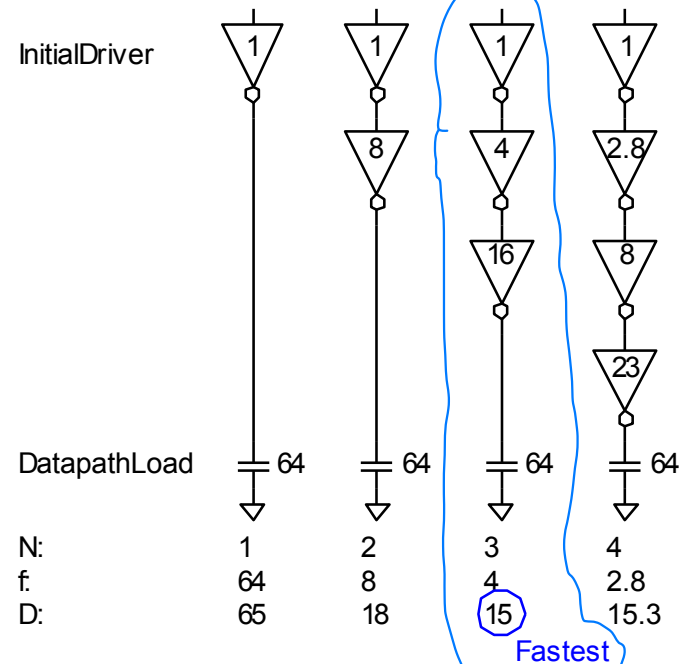

# Derivation

- Consider adding inverters to end of path
  - How many give least delay?

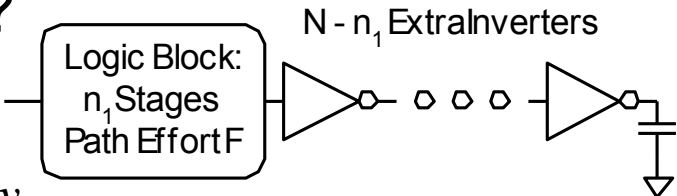
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$


The diagram shows a logic block labeled "Logic Block: n<sub>1</sub> Stages Path Effort F" connected to a series of inverters. The first inverter is connected to the logic block, and the last inverter is connected to ground. The text "N - n<sub>1</sub> Extra Inverters" is written above the chain of inverters.

$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort  $\rho = F^{\frac{1}{N}}$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$

 


# Best Stage Effort

- ❑  $p_{inv} + \rho(1 - \ln \rho) = 0$  has no closed-form solution
- ❑ Neglecting parasitics ( $p_{inv} = 0$ ), we find  $\rho = 2.718$  (e)
- ❑ For  $p_{inv} = 1$ , solve numerically for  $\rho = 3.59$


 
# Sensitivity Analysis

- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$  gives delay within 15% of optimal
  - We can be sloppy!
  - I like  $\rho = 4$

# Example, Revisited


- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- ❑ Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs  $A[3:0]$
- Each input may drive 10 unit-sized transistors

- ❑ Ben needs to decide:

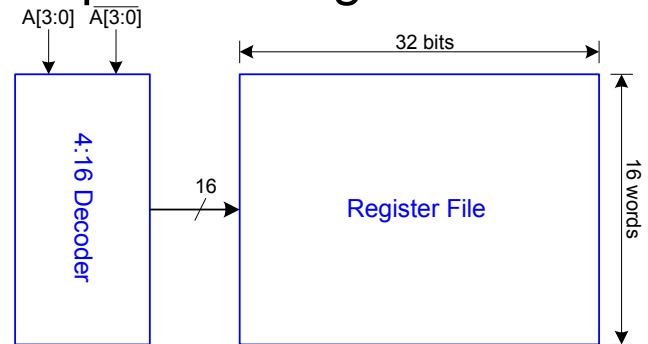- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



# Number of Stages

- ❑ Decoder effort is mainly electrical and branching

Electrical Effort:  $H =$

Branching Effort:  $B =$

- ❑ If we neglect logical effort (assume  $G = 1$ )

Path Effort:  $F =$

Number of Stages:  $N =$

# Number of Stages

- ❑ Decoder effort is mainly electrical and branching

Electrical Effort:  $H = (32 \cdot 3) / 10 = 9.6$

Branching Effort:  $B = 8$

- ❑ If we neglect logical effort (assume  $G = 1$ )

Path Effort:  $F = GBH = 76.8$

Number of Stages:  $N = \log_4 F = 3.1$

- ❑ Try a 3-stage design

# Gate Sizes & Delay


Logical Effort:  $G =$

Path Effort:  $F =$

Stage Effort:  $\hat{f} =$

Path Delay:  $D =$ 

Gate sizes:  $z =$
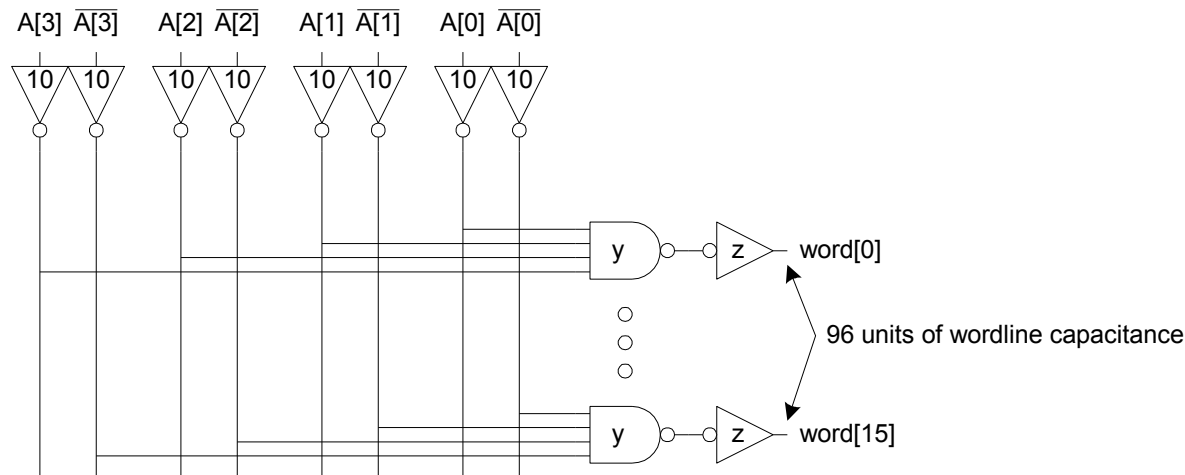
$$y =$$


# Gate Sizes & Delay


Logical Effort:  $G = 1 * 6/3 * 1 = 2$

Path Effort:  $F = GBH = 154$


Stage Effort:  $\hat{f} = F^{1/3} = 5.36$

Path Delay:  $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

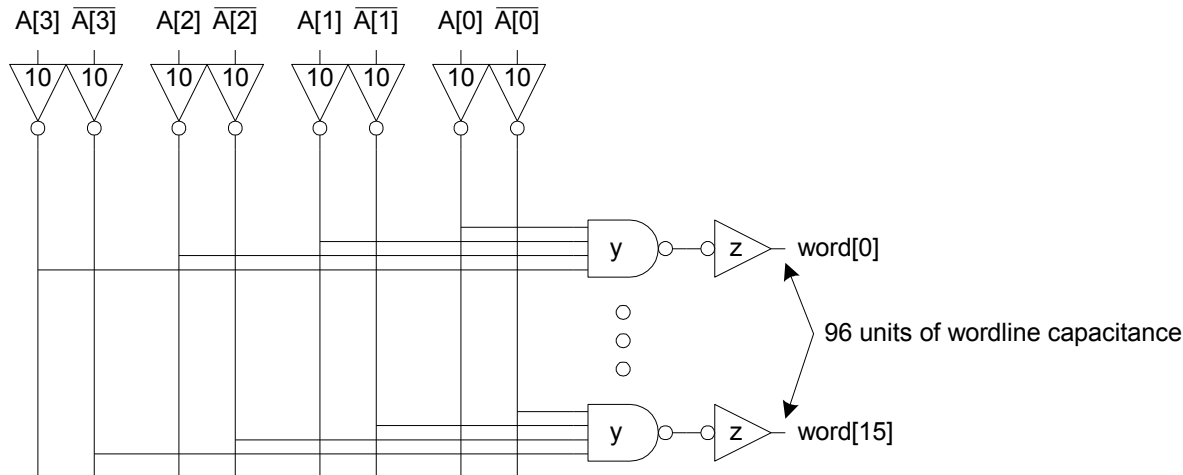Gate sizes:  $z = 96 * 1/5.36 = 18$      $y = 18 * 2/5.36 = 6.7$



# 74154 Decoder

 

# Comparison

- ❑ Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6



# Review of Definitions

Term	Stage	Path
number of stages	1	$N$
logical effort	$g$	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$
branching effort	$b = \frac{C_{\text{on-path}} + C_{\text{off-path}}}{C_{\text{on-path}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	$f$	$D_F = \sum f_i$
parasitic delay	$p$	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

# Method of Logical Effort

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort
- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


# Limits of Logical Effort

- ❑ Chicken and egg problem
  - Need path to compute  $G$
  - But don't know number of stages without  $G$
- ❑ Simplistic delay model
  - Neglects input rise time effects
- ❑ Interconnect
  - Iteration required in designs with wire
- ❑ Maximum speed only
  - Not minimum area/power for constrained delay


# Summary

- ❑ Logical effort is useful for thinking of delay in circuits
  - Numeric logical effort characterizes gates
  - NANDs are faster than NORs in CMOS
  - Paths are fastest when effort delays are  $\sim 4$
  - Path delay is weakly sensitive to stages, sizes
  - But using fewer stages doesn't mean faster paths
  - Delay of path is about  $\log_4 F$  FO4 inverter delays
  - Inverters and NAND2 best for driving large caps
- ❑ Provides language for discussing fast circuits
  - But requires practice to master


# Decoder with one polarity of input

 

# A path with different logical and electrical efforts

 

**Fig. 3.29** Resistance for inputs  
 “110”, “111”, “001”, “000”,  
 “100”

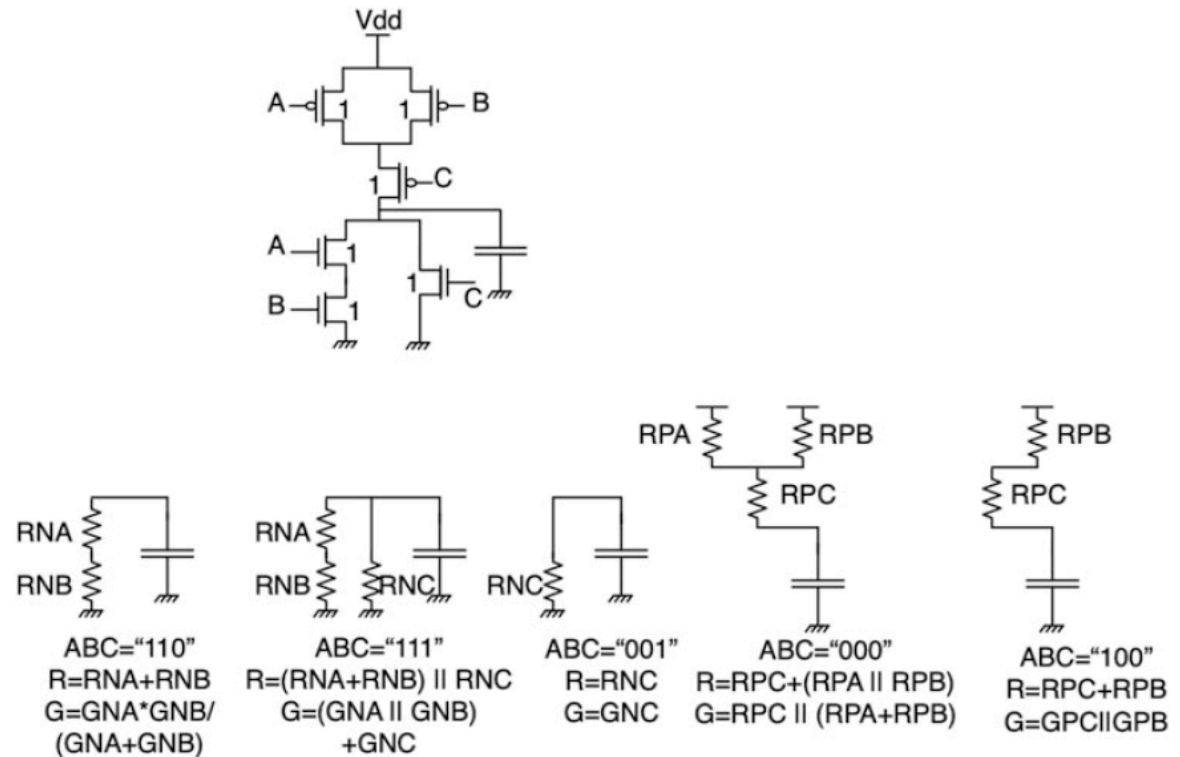

mate of the path effort by assuming the logical effort is unity. The electrical effort is  $32 \times 3/10 = 9.6$ . The branching effort is 8 because the true and complement address inputs each control half of the outputs. Path effort is  $9.6 \times 8 = 76.8$ . Hence, we should use about  $\log_4 76.8 = 3.1$  stages. Because we neglected logical effort, the actual number of stages will be slightly higher than the number we have estimated. Figure 2.2 shows a three-stage circuit, while Exercise 2.3 considers a four-stage circuit.

The three-stage circuit uses 16 four-input NAND gates. Because each address input must drive eight of the NAND gates, yet can handle only a relatively small input capacitance, we use an inverter to power up the signal. How do we size the decoder, and what is its delay?

Because the logical effort is  $1 \times 2 \times 1 = 2$ , the actual path effort is 154 and the stage effort is  $f = (154)^{1/3} = 5.36$ . Working from the output, the final inverter must have input capacitance  $z = (32 \times 3) \times 1/5.36 = 18$ , and the NAND gate must have input capacitance  $y = 18 \times 2/5.36 = 6.7$ . The delay is  $3f + P =$