

Partition of Large Combinational Circuits

 Rule: To reduce test generation costs and/or test application time



 


邏輯冗余

Logic Redundancy


Rule: Avoid or eliminate redundancy ckt.

 - Design errors
- Undetectable faults
- Invalidation of some tests有些 test是无效?
- Bias fault coverage fault coverage 会变低




Global Feedback Paths

Rule: break global feedback

 


Scan System


Pass mode

 

Original design

 

Scan System

 


Original design

Modified circuit


Scan System

 - Long test time 空學縣
- Large test data
- Too much overhead
- How to test DFT circuit itself




Scan System Performance

 
- How to calculate the test cycle:
 - L: Length of scan chain, Npattern: Number of test patterns



 - Example: Apply 5000 test patterns to a CUT with 10000 SFF
 - Total cycles = 50015000 cycles (5000+1)x10000 shift cycles + 5000 capture cycles






 

m SCAN 电路

Example

 


load		capture		unload	
CK=PPPP	:7%洋兒灣	り記され PECK=P ASTICION	为对思想果讀	CK=PPPP	
SE=1111	SE $1 \rightarrow 0^3$	SE=0	>	SE=1111	
SI=X011	→ 为署判fi	nults		SO=HIXX	到 high,就是
PI=1	PO=L ₀ _W	= 0			

在第5个clock

PO及SO有限考慮正常新光


Scan DFT Overhead

 - Performance Degradation
- Design overhead
- Hardware overhead
- Yield loss
- Power overhead




Example-Normal Mode


?有問題的地方

 


Example-Test Mode

 


Full Serial Integrated Scan

 


Isolated Serial Scan (Scan/set)

 

Full Isolated Scan (Structured)

 

 
Random-Access Scan (Non serial-structured)



不用删順序存data

- High area overhead
- Faster test application: only bit change
- Concept of crosscheck

 Random-Access Scan (Non serial-structured)




Scan Cell Design

- Static / Dynamic
- Single / Double stages
- Latch / Flip-flop (Clocking Scheme)

Usually Two Operation Modes

- Functional mode
- Shift mode

IBM LSSD Scan Cell

 

IBM LSSD Scan Cell

Advantages


- It allows us to insert scan into a latchbased design.
- LSSD is guaranteed to be race free, which not case for the Muxed-D and Clocked-scan design.


Disadvantages

 It requires routing for the additional clocks, which increases routing complexity.

IBM LSSD Scan Cell (Cont.)


Switch / Inverter level

 

 


Clocking Scheme of LSSD Double-Latch

non-overlapping: avoid skew

 


 LSSD <u>Single-Latch</u> Design latch 鱼薛琦到output, 讓愛科州達送出






Example

 

Scan Design Costs

- Area overhead
- Possible performance degradation
- Extra pins
- High test time
- Extra clock control

More Area OverHead

 


Advanced Scan Concepts

- Partial scan (P.S.):有些变 scan register.有些不用
- Multiple test session (M.T.S.): 「scan chain 治成多段
- Multiple scan chains (M.S.C.) 多例 input
- Broadcast scan chains (B.S.C)

Method	P.S.	M.T.S.	M.S.C.	B.S.C.
Area overhead	*	same	same or	same
Performance Degradation	*	same	same	same
Extra pins	same	same	same or	—
Extra clock control	same	same	same	same
Test application time	V or ∱	Y	*	\

 Partial Scan: Only a subset of all flip-flops are scanned




- Trade-off between
 - -Area overhead
 - -Test generation complexity


Partial Scan and Full Scan

- Full scan
 - -- Every flip-flop is scanable
 - -- More hardware overhead
 - -- Higher fault coverage
 - -- Longer test time:所有电路都事美
 - -- Shorter ATPG time required 答题則
- Partial scan
 - -- Not every flip-flop is scanable
 - -- Less hardware overhead
 - -- Less fault coverage
 - -- Shorter test time
 - -- Longer ATPG time required


Scan Design Flow

 

Scan Register Selection

 

Clock Skew Between Two Clock Domains

 

Lock-up Latch

