

# **Introduction to CMOS VLSI Design**

## **Lecture 3: CMOS Transistor Theory**

# Outline

---

- ☐ Introduction
- ☐ MOS Capacitor
- ☐ nMOS I-V Characteristics
- ☐ pMOS I-V Characteristics
- ☐ Gate and Diffusion Capacitance
- ☐ Pass Transistors
- ☐ RC Delay Models

$$Q = C * V$$

電荷量


電容

電圧




$$I = \frac{Q}{\Delta t} = \frac{C * \Delta V}{\Delta t} \Rightarrow \Delta t = \frac{C}{I} * \Delta V$$
 
# Introduction

- ❑ So far, we have treated transistors as ideal switches
- ❑ An ON transistor passes a finite amount of current
  - Depends on terminal voltages
  - Derive current-voltage (I-V) relationships
- ❑ Transistor gate, source, drain all have capacitance
  - $I = C (\Delta V / \Delta t) \rightarrow \Delta t = (C / I) \Delta V$
  - Capacitance and current determine speed
- ❑ Also explore what a “degraded level” really means





电容 C 符号

   

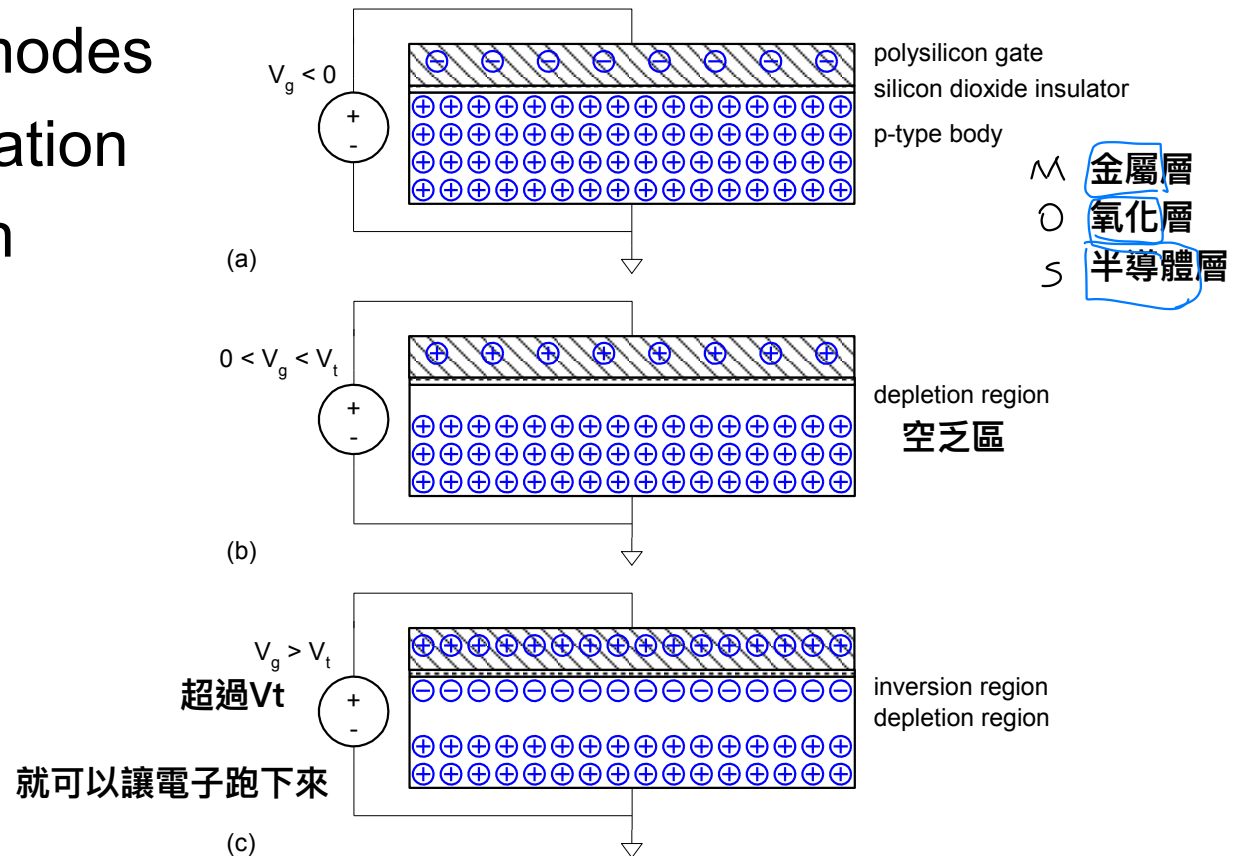 
# MOS Capacitor

- ❑ Gate and body form MOS capacitor
- ❑ Operating modes
  - Accumulation
  - Depletion
  - Inversion


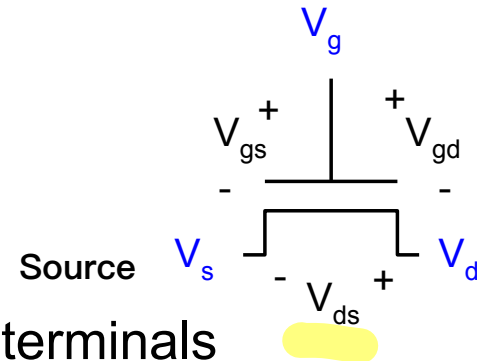
# Terminal Voltages

- ❑ Mode of operation depends on  $V_g$ ,  $V_d$ ,  $V_s$ 
  - $V_{gs} = V_g - V_s$
  - $V_{gd} = V_g - V_d$
  - $V_{ds} = V_d - V_s = V_{gs} - V_{gd}$
- ❑ Source and drain are symmetric diffusion terminals
  - By convention, source is terminal at lower voltage
  - Hence  $V_{ds} \geq 0$
- ❑ nMOS body is grounded. First assume source is 0 too.
- ❑ Three regions of operation
  - *Cutoff*
  - *Linear*
  - *Saturation*




# nMOS Cutoff

❑ No channel

❑  $I_{ds} = 0$

正導通

截止區  
都不會流動


 


要吸夠多電子過去 才會導通

# nMOS Linear

- ❑ Channel forms
- ❑ Current flows from d to s
  - $e^-$  from s to d
- ❑  $I_{ds}$  increases with  $V_{ds}$
- ❑ Similar to linear resistor

線性區

  

电子流

n p

n p n



电流⊕ 电子流⊖

正常是 S → D 电子流的流向  
source drain


逆偏



# nMOS Saturation

- ❑ Channel pinches off
- ❑  $I_{ds}$  independent of  $V_{ds}$
- ❑ We say current saturates
- ❑ Similar to current source

飽和區  
電流固定


 


# I-V Characteristics

- ❑ In Linear region,  $I_{ds}$  depends on
  - How much charge is in the channel?
  - How fast is the charge moving?
  
# Channel Charge

- ❑ MOS structure looks like parallel plate capacitor while operating in inversion
  - Gate – oxide – channel
- ❑  $Q_{\text{channel}} =$



$$C = \sum_{\substack{L \\ \downarrow \\ E_{ox}}} \frac{1}{d} f_{ox}$$

Diagram of a MOSFET structure showing the source (S), gate (G), and drain (D) regions. The source is labeled "S nt" and the drain is labeled "D nk". The gate is labeled "G". The channel region is labeled "e-e-c-e-e". The gate voltage is  $V_{gs}$  and the drain voltage is  $V_{gd}$ . The source voltage is  $V_{ss}$ . The channel length is  $L$  and the channel width is  $W$ . The channel is divided into segments of length  $L/4$  and  $L/2$ . The channel is divided into segments of length  $L/4$  and  $L/2$ . The channel is divided into segments of length  $L/4$  and  $L/2$ .



$$V = V_{gc} - V_t = \frac{V_{gs} + V_{gd}}{2} - V_t$$

$$= V_{gs} - \frac{V_{gs} - V_{gd}}{2} - V_t$$

$$= V_{gs} - \frac{V_{gs} - V_{gd}}{2} - V_t$$
  
# Channel Charge

- ❑ MOS structure looks like parallel plate capacitor while operating in inversion
  - Gate – oxide – channel
- ❑  $Q_{\text{channel}} = CV$
- ❑  $C =$



# Channel Charge



- ❑ MOS structure looks like parallel plate capacitor while operating in inversion
  - Gate – oxide – channel

- ❑  $Q_{\text{channel}} = CV$

- ❑  $C = C_g = \epsilon_{\text{ox}} WL / t_{\text{ox}} = C_{\text{ox}} WL$

$$C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$$

- ❑  $V =$

  

# Channel Charge



- ❑ MOS structure looks like parallel plate capacitor while operating in inversion
  - Gate – oxide – channel

- ❑  $Q_{\text{channel}} = CV$

- ❑  $C = C_g = \epsilon_{\text{ox}} WL / t_{\text{ox}} = C_{\text{ox}} WL$


$$C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$$

  - ❑  $V = V_{gc} - V_t = (V_{gs} - V_{ds}/2) - V_t$


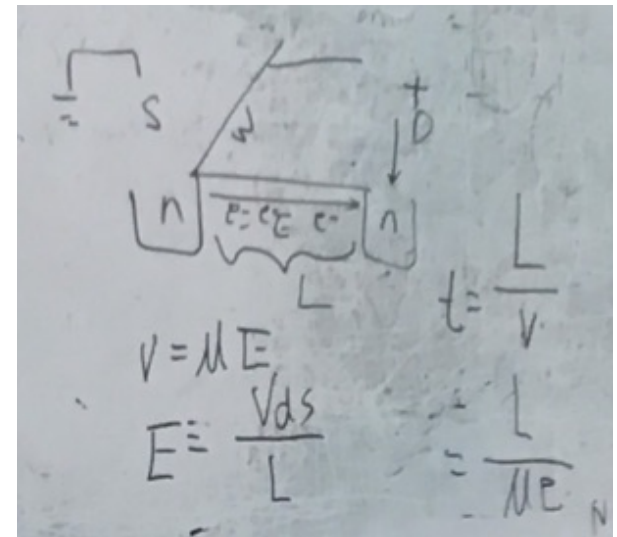
# Carrier velocity

- ❑ Charge is carried by e-
- ❑ Carrier velocity  $v$  proportional to lateral E-field between source and drain
- ❑  $v = \mu E$                        $\mu$  called mobility
- ❑  $E = V_{ds}/L$
- ❑ Time for carrier to cross channel:
  - $t = L / v$





# nMOS Linear I-V

□ Now we know

- How much charge  $Q_{\text{channel}}$  is in the channel
- How much time  $t$  each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$= \beta \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$\beta = \mu C_{\text{ox}} \frac{W}{L}$$

$$I = \frac{Q_{\text{channel}}}{t}$$

$$= \frac{C V}{t} = \frac{C_{\text{ox}} W \left[ \left( V_{\text{gs}} - \frac{V_{\text{ds}}}{2} \right) - V_t \right] \mu C_{\text{ox}} W}{L} V_{\text{ds}}$$

$$V_{\text{ds}} = V_{\text{gs}} - V_{\text{gd}}$$

② ①
①
②

↓

# nMOS Saturation I-V

- ❑ If  $V_{gd} < V_t$ , channel pinches off near drain
  - When  $V_{ds} > V_{dsat} = V_{gs} - V_t$
- ❑ Now drain voltage no longer increases current

$$I_{ds} =$$

# nMOS Saturation I-V

- ❑ If  $V_{gd} < V_t$ , channel pinches off near drain
  - When  $V_{ds} > V_{dsat} = V_{gs} - V_t$
- ❑ Now drain voltage no longer increases current

$$I_{ds} = \beta \left( V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat}$$

# nMOS Saturation I-V

- ❑ If  $V_{gd} < V_t$ , channel pinches off near drain
  - When  $V_{ds} > V_{dsat} = V_{gs} - V_t$
- ❑ Now drain voltage no longer increases current


$$\begin{aligned} I_{ds} &= \beta \left( V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat} \\ &= \frac{\beta}{2} (V_{gs} - V_t)^2 \end{aligned}$$

# nMOS Saturation I-V

- ❑ If  $V_{gd} < V_t$ , channel pinches off near drain
  - When  $V_{ds} > V_{dsat} = V_{gs} - V_t$
- ❑ Now drain voltage no longer increases current

$$I_{ds} = \beta \left( V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat}$$

$$= \frac{\beta}{2} (V_{gs} - V_t)^2$$

 

$$\frac{(V_{GS} - V_t)(V_{GS} - V_t)}{2}$$


# nMOS I-V Summary

□ Shockley 1<sup>st</sup> order transistor models

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$
 
# Example

- ❑ We will be using a  $0.6\text{ }\mu\text{m}$  process for your project
  - From AMI Semiconductor
  - $t_{\text{ox}} = 100\text{ }\text{\AA}$
  - $\mu = 350\text{ cm}^2/\text{V}\cdot\text{s}$
  - $V_t = 0.7\text{ V}$
- ❑ Plot  $I_{\text{ds}}$  vs.  $V_{\text{ds}}$ 
  - $V_{\text{gs}} = 0, 1, 2, 3, 4, 5$
  - Use  $W/L = 4/2\lambda$



$$\beta = \mu C_{\text{ox}} \frac{W}{L} = (350) \left( \frac{3.9 \cdot 8.85 \cdot 10^{-14}}{100 \cdot 10^{-8}} \right) \left( \frac{W}{L} \right) = 120 \frac{W}{L} \mu\text{A}/\text{V}^2$$



# pMOS I-V


- ❑ All dopings and voltages are inverted for pMOS
- ❑ Mobility  $\mu_p$  is determined by holes
  - Typically 2-3x lower than that of electrons  $\mu_n$
  - 120 cm<sup>2</sup>/V\*s in AMI 0.6  $\mu$ m process
- ❑ Thus pMOS must be wider to provide same current
  - In this class, assume  $\mu_n / \mu_p = 2$
  - \*\*\* plot I-V here

# Capacitance

- ❑ Any two conductors separated by an insulator have capacitance
- ❑ Gate to channel capacitor is very important
  - Creates channel charge necessary for operation
- ❑ Source and drain have capacitance to body
  - Across reverse-biased diodes
  - Called diffusion capacitance because it is associated with source/drain diffusion

 
# Gate Capacitance

- Approximate channel as connected to source
- $C_{gs} = \epsilon_{ox} WL / t_{ox} = C_{ox} WL = C_{permicron} W$
- $C_{permicron}$  is typically about 2 fF/ $\mu\text{m}$



 
# Diffusion Capacitance

- ❑  $C_{sb}$ ,  $C_{db}$
- ❑ Undesirable, called *parasitic* capacitance
- ❑ Capacitance depends on area and perimeter
  - Use small diffusion nodes
  - Comparable to  $C_g$  for contacted diff
  - $\frac{1}{2} C_g$  for uncontacted
  - Varies with process


 
# Pass Transistors

- ❑ We have assumed source is grounded
- ❑ What if source  $> 0$ ?
  - e.g. pass transistor passing  $V_{DD}$




# Pass Transistors

- ❑ We have assumed source is grounded

- ❑ What if source  $> 0$ ?

  - e.g. pass transistor passing  $V_{DD}$

 

- ❑  $V_g = V_{DD}$

  - If  $V_s > V_{DD} - V_t$ ,  $V_{gs} < V_t$

  - Hence transistor would turn itself off





- ❑ nMOS pass transistors pull no higher than  $V_{DD} - V_{tn}$

  - Called a degraded “1”



  - Approach degraded value slowly (low  $I_{ds}$ )

- ❑ pMOS pass transistors pull no lower than  $V_{tp}$



# Pass Transistor Ckts

    

# Pass Transistor Ckts

  

注意 這裡不會重複減

  

這種就會重複減到





# Effective Resistance

- ❑ Shockley models have limited value
  - Not accurate enough for modern transistors
  - Too complicated for much hand analysis
- ❑ Simplification: treat transistor as resistor
  - Replace  $I_{ds}(V_{ds}, V_{gs})$  with effective resistance  $R$ 
    - $I_{ds} = V_{ds}/R$
  - $R$  averaged across switching of digital gate
- ❑ Too inaccurate to predict current at any given time
  - But good enough to predict RC delay
 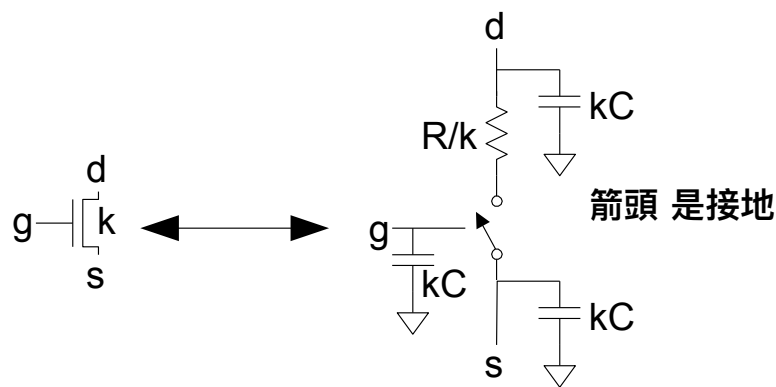
# RC Delay Model

- ❑ Use equivalent circuits for MOS transistors
  - Ideal switch + capacitance and ON resistance
  - Unit nMOS has resistance  $R$ , capacitance  $C$
  - Unit pMOS has resistance  $2R$ , capacitance  $C$
- ❑ Capacitance proportional to width
- ❑ Resistance inversely proportional to width




# RC Values

- ❑ Capacitance
  - $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$  of gate width
  - Values similar across many processes
- ❑ Resistance
  - $R \approx 6 \text{ K}\Omega \cdot \mu\text{m}$  in  $0.6\mu\text{m}$  process
  - Improves with shorter channel lengths
- ❑ Unit transistors
  - May refer to minimum contacted device ( $4/2 \lambda$ )
  - Or maybe  $1 \mu\text{m}$  wide device
  - Doesn't matter as long as you are consistent
 
# Inverter Delay Estimate

- Estimate the delay of a fanout-of-1 inverter




- ❑ Estimate the delay of a fanout-of-1 inverter



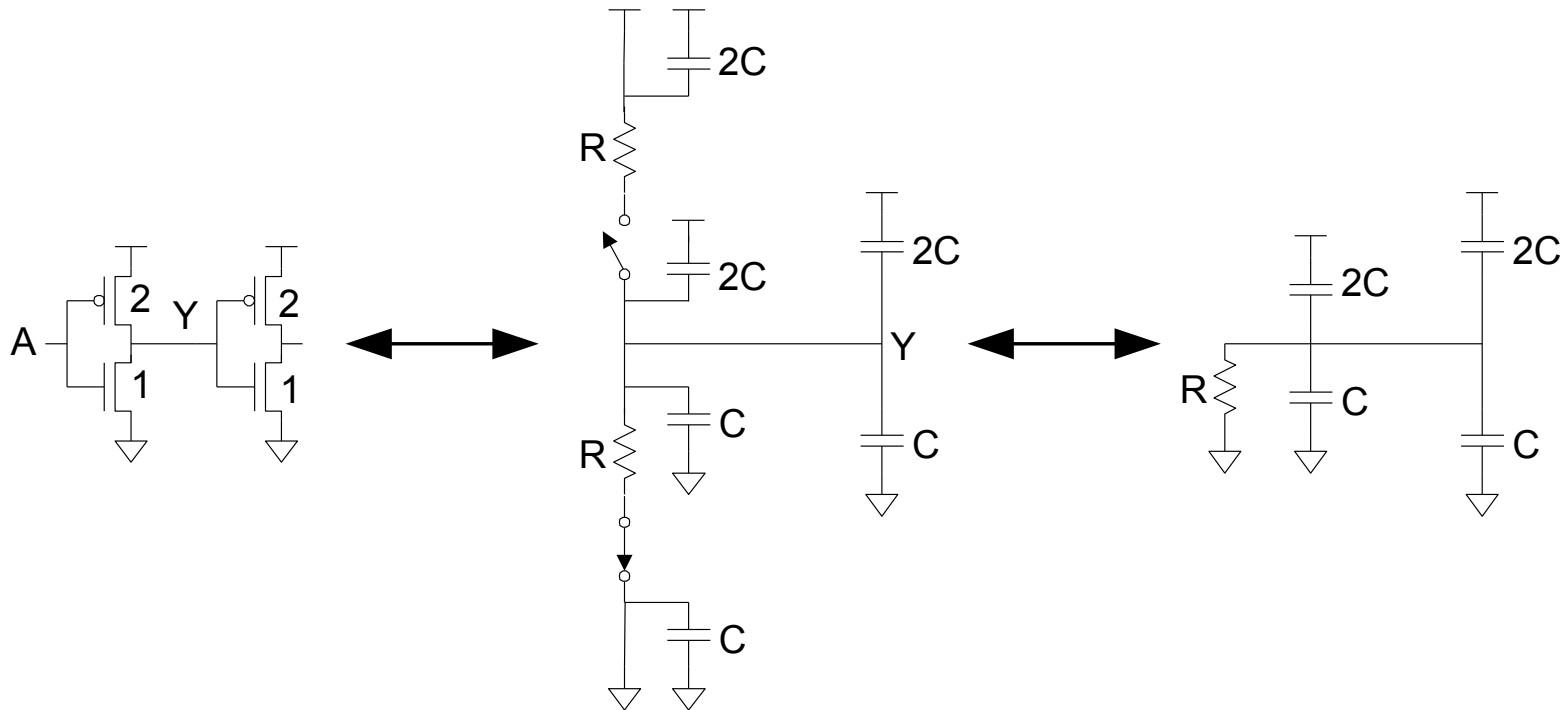
# Inverter Delay Estimate

- Estimate the delay of a fanout-of-1 inverter


 
# Inverter Delay Estimate

- Estimate the delay of a fanout-of-1 inverter



$$d = 6RC$$